

COMPUTER SYSTEMS AND ORGANIZATION

Part 1

Khyati Kiyawat

Daniel G. Graham PhD

September 11, 2023




UNIVERSITY
of VIRGINIA

ENGINEERING

REVIEW

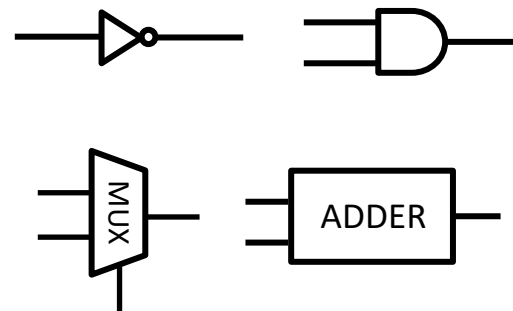
- ✓ What are logic gates?
- ✓ How to make circuits like Multiplexers, Adders?
- ✓ How to represent numbers in different formats?
- ✓ How to store data in registers?





Binary: 0110 Hex:0xAF23

CLOCKS EDGES


Rising Edge (Also called positive edge)

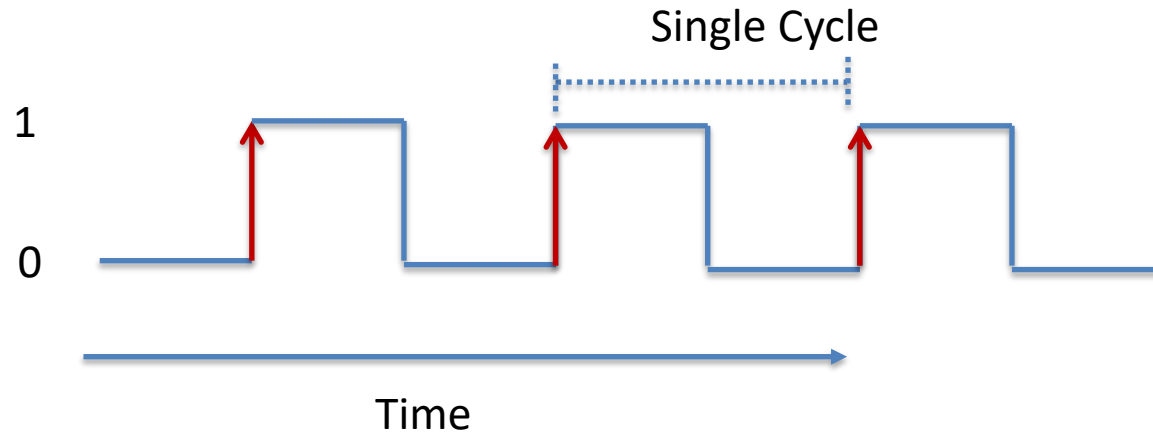

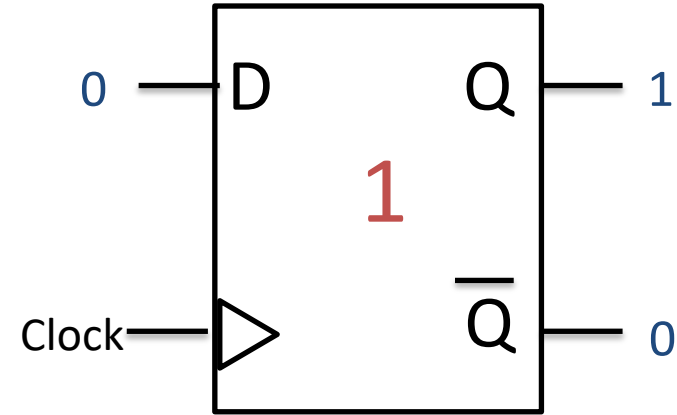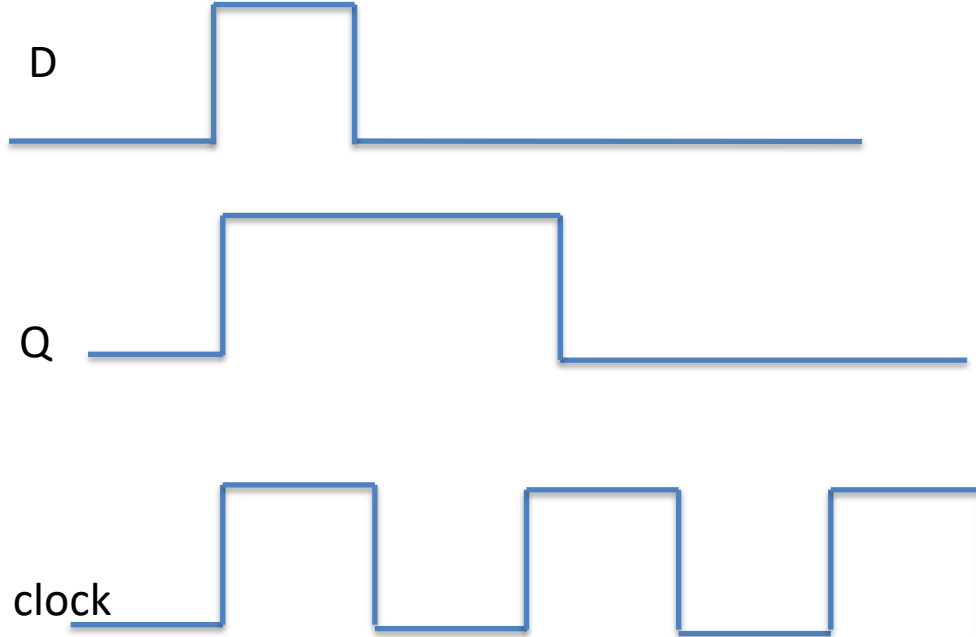THE FLIP FLOP HOLD HOLDS THE VALUE FOR A CLOCK CYCLE



BUILDING A REGISTER FROM FLIP FLOPS

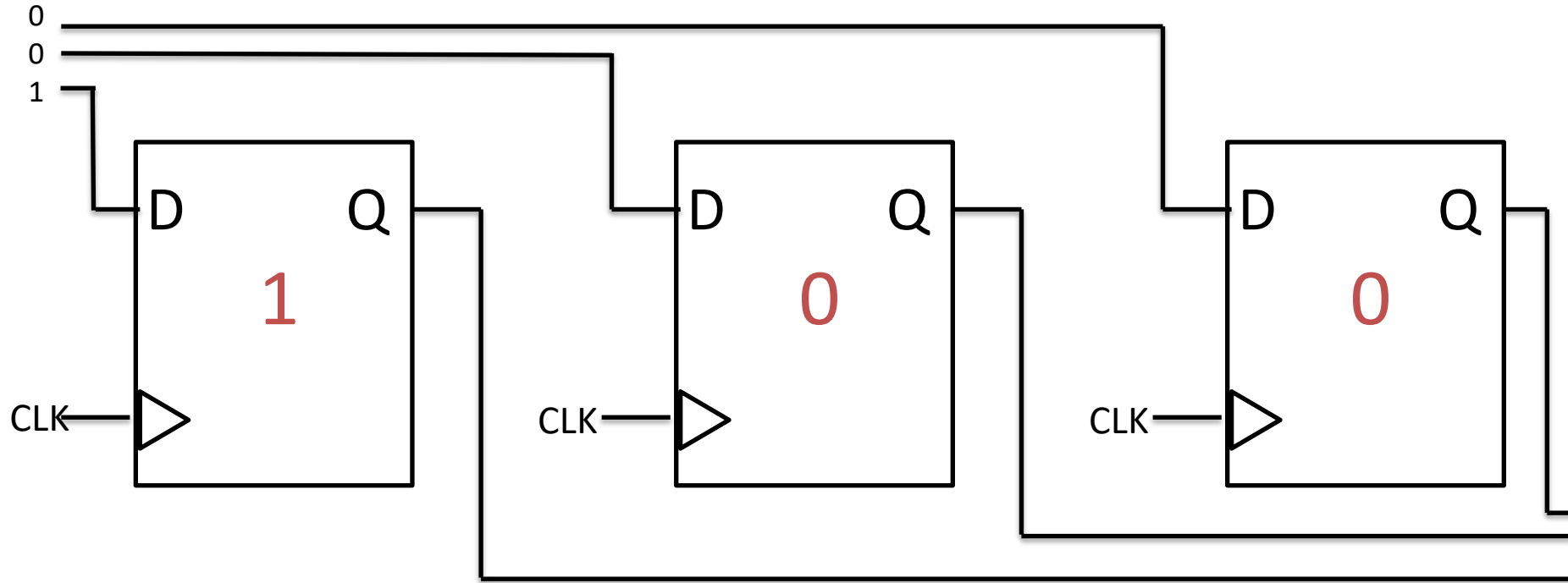


Removed Q (bar) for reability

3-BIT COUNTER

Let's put it all together and build a 3-bit counter

Circuit that counts from

000,
001,
010,
011,
100,
101,
110,
111

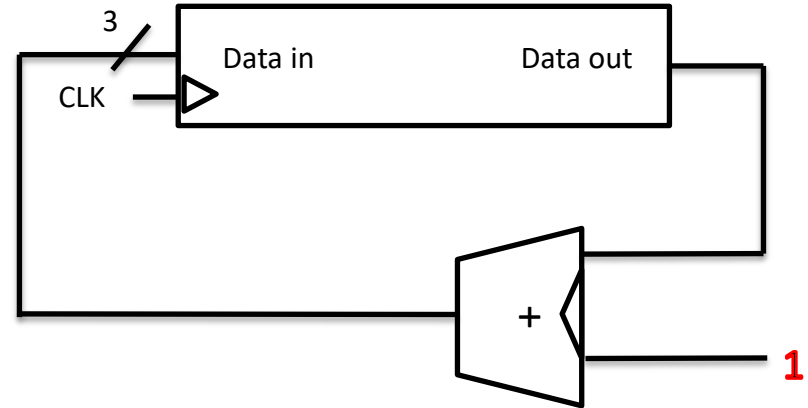


TODAY'S LECTURE

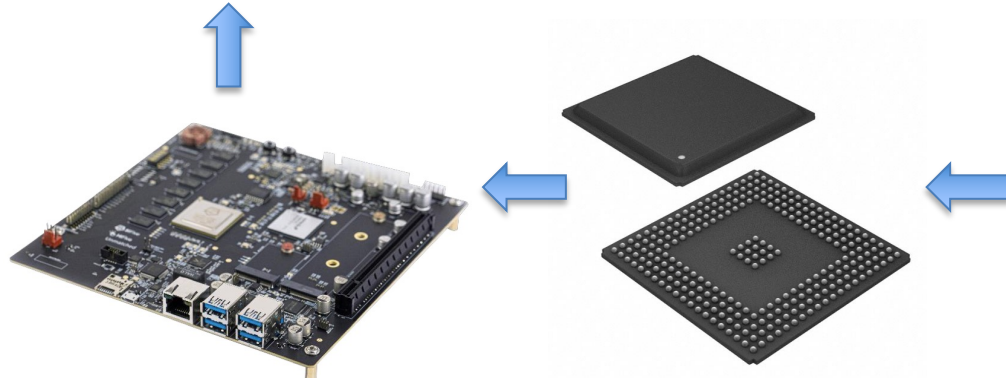1. How do we use registers as building block to design a computer?
2. What is a register file and how to implement it?
3. Other memory components


The diagram illustrates the abstraction process in three stages:

- A physical component (a black integrated circuit) is shown inside a blue circle.
- A blue arrow points to a logic gate representation (an AND gate) with inputs \hat{A} and B , and output Y .
- A second blue arrow points to a Petri net representation (a V-shaped transition) with input places F and A , output places D and R , and a label B above the transition.




8


MEMORY COMPONENTS OF A PROCESSOR

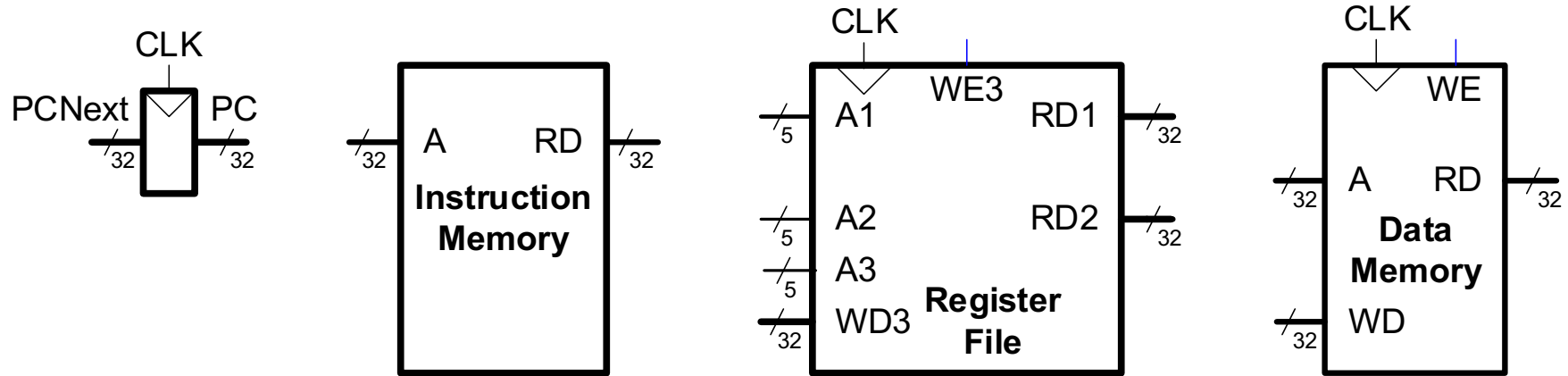

PROGRAM COUNTER

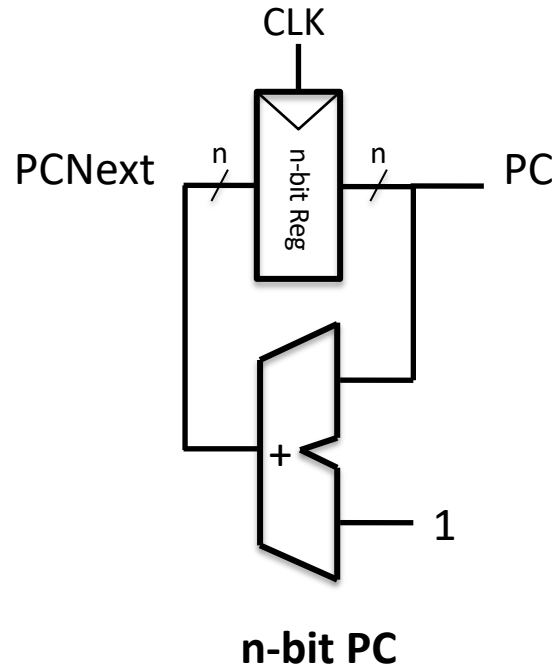


- To track where we are in a program

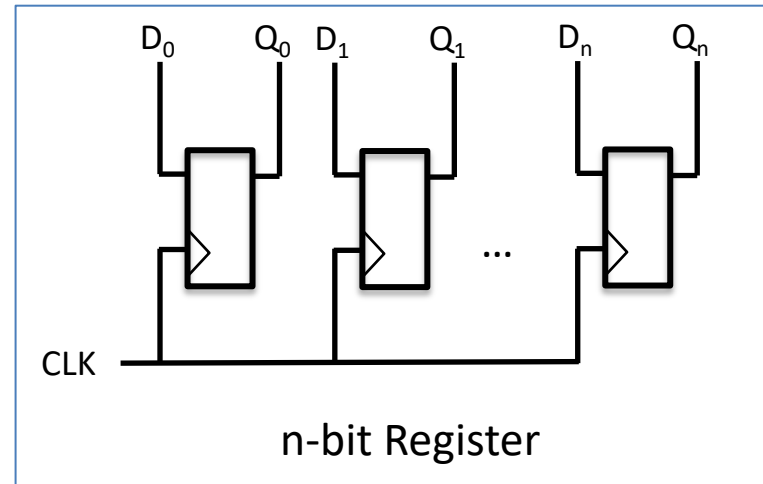


REGISTER FILE

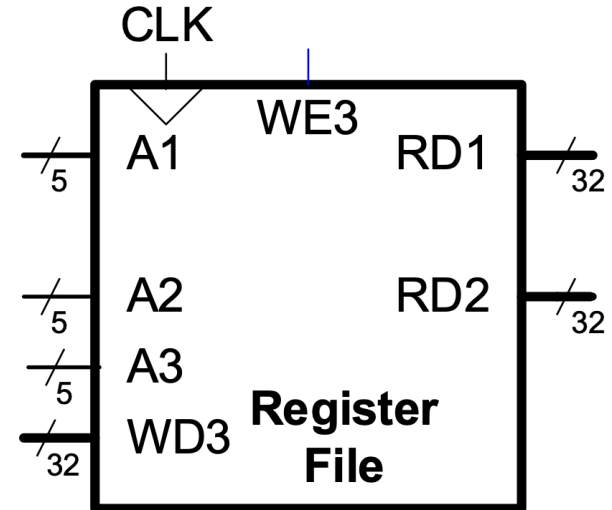- Temporary storage location
- Stores immediately needed variables




LET'S BUILD A REGISTER FILE OF FOUR REGISTERS

READ FROM A REGISTER FILE

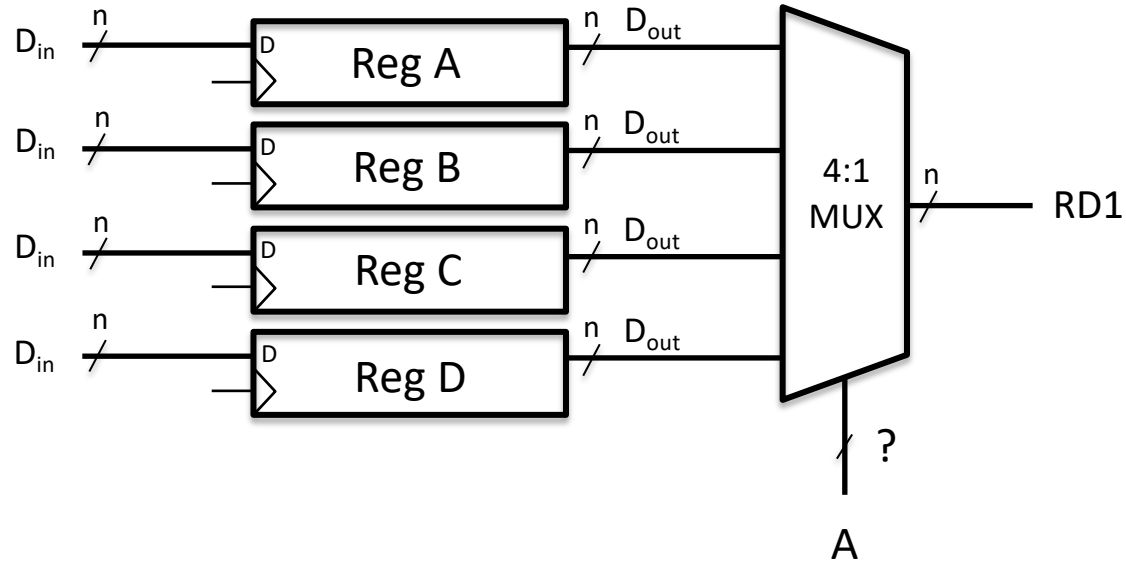


READ FROM A REGISTER FILE

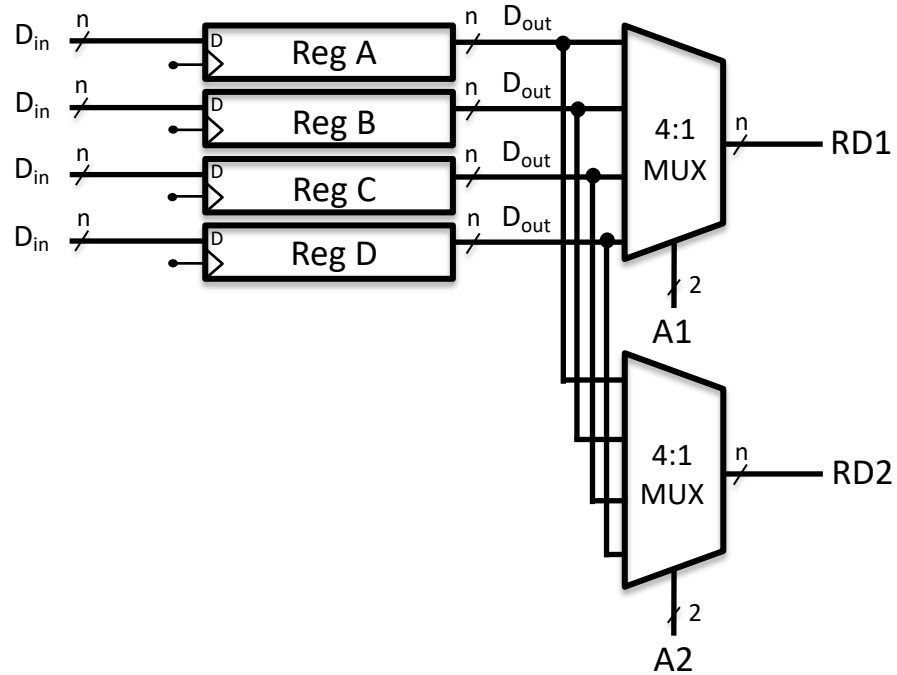

WRITE TO A REGISTER FILE

We want to write to a particular register.


Do you see a problem with this circuit?

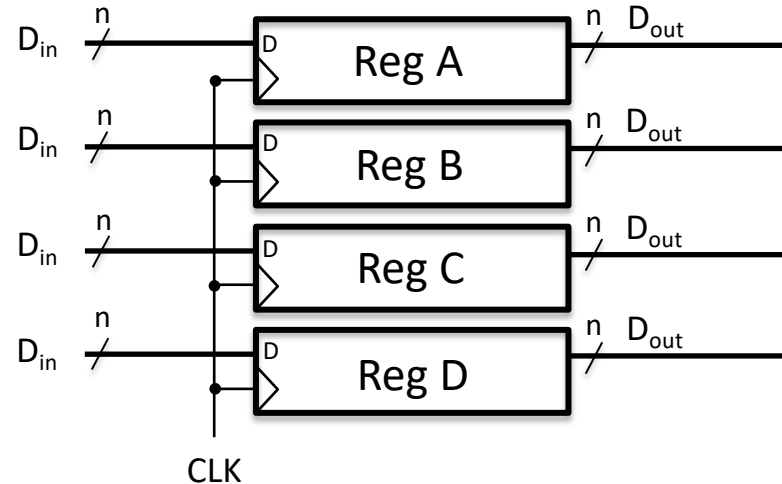


WRITE TO A REGISTER FILE

Additional input signals:

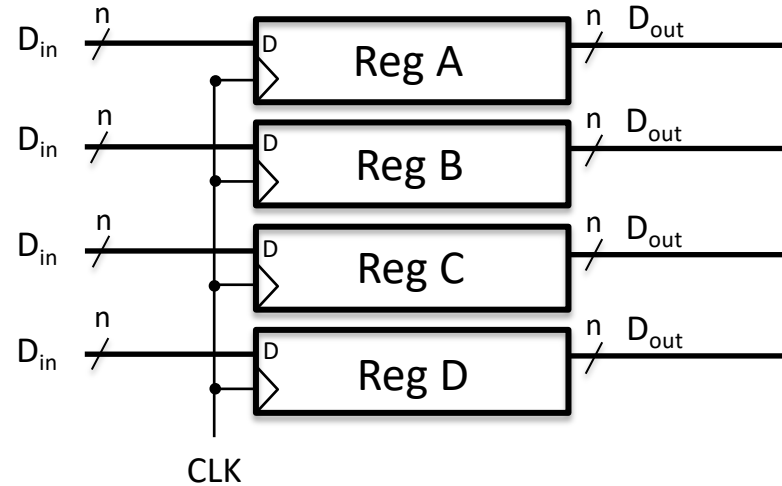1. Write enable
2. Address of the register to be written (A3)




WRITE TO A REGISTER FILE

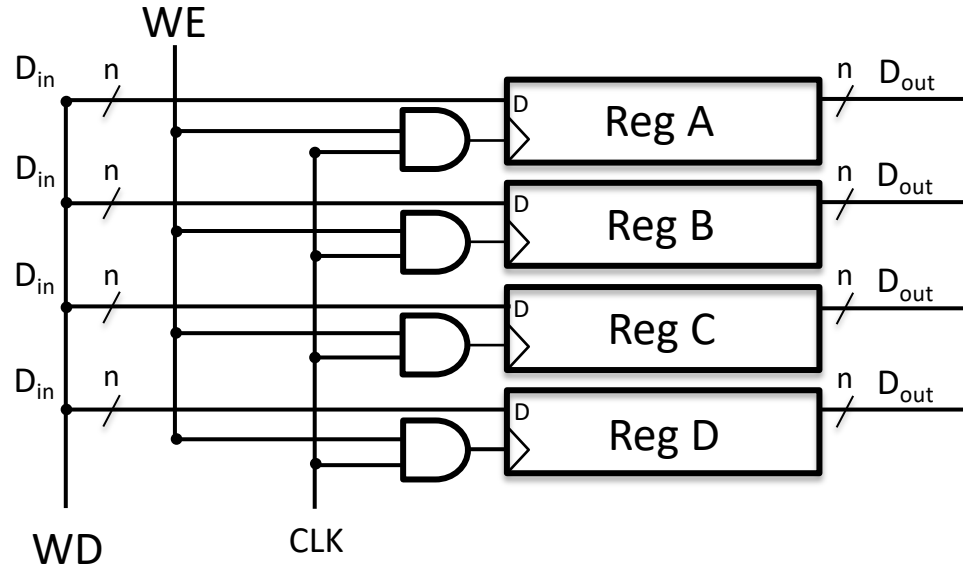

Are we missing
a component?


DEMULTIPLEXER (DEMUX)

Example: 1:2 Demux

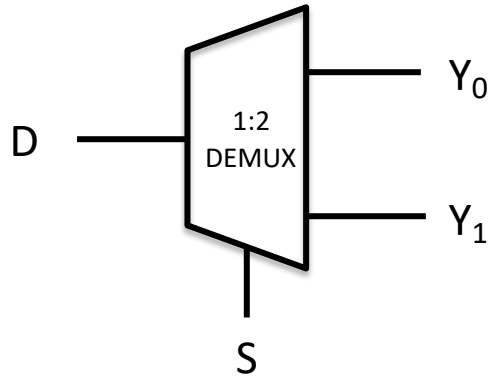


S	Y0	Y1
0	D	0
1	0	D

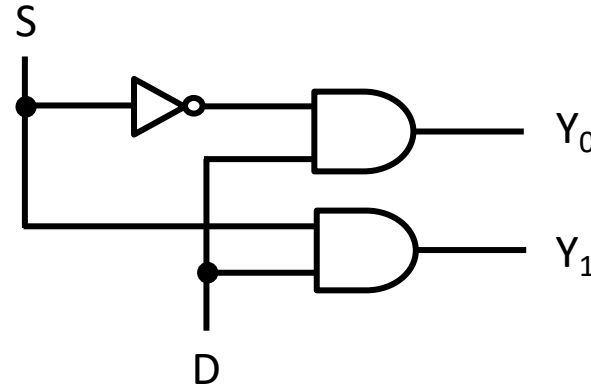- Connects one input to one of the **N** outputs
- **Select** input is $\log_2 N$ bits – control input




HIGH-ORDER DEMULTIPLEXER

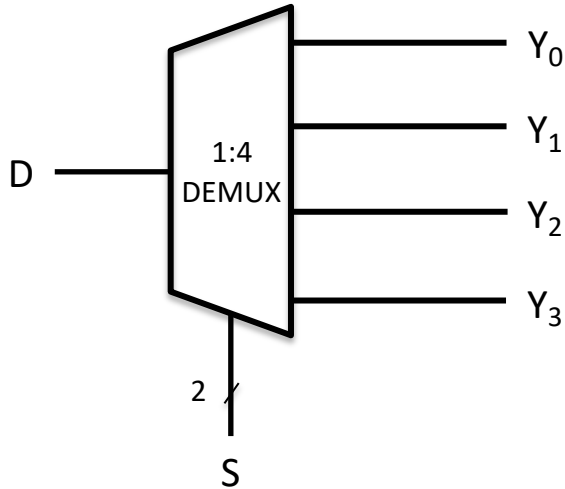


S	Y0	Y1	Y2	Y3
00	D	0	0	0
01	0	D	0	0
10	0	0	D	0
11	0	0	0	D

Can you implement higher-order demuxes like 1:8, 1:16, 1:64 using lower-order demuxes?

WRITE TO A REGISTER FILE

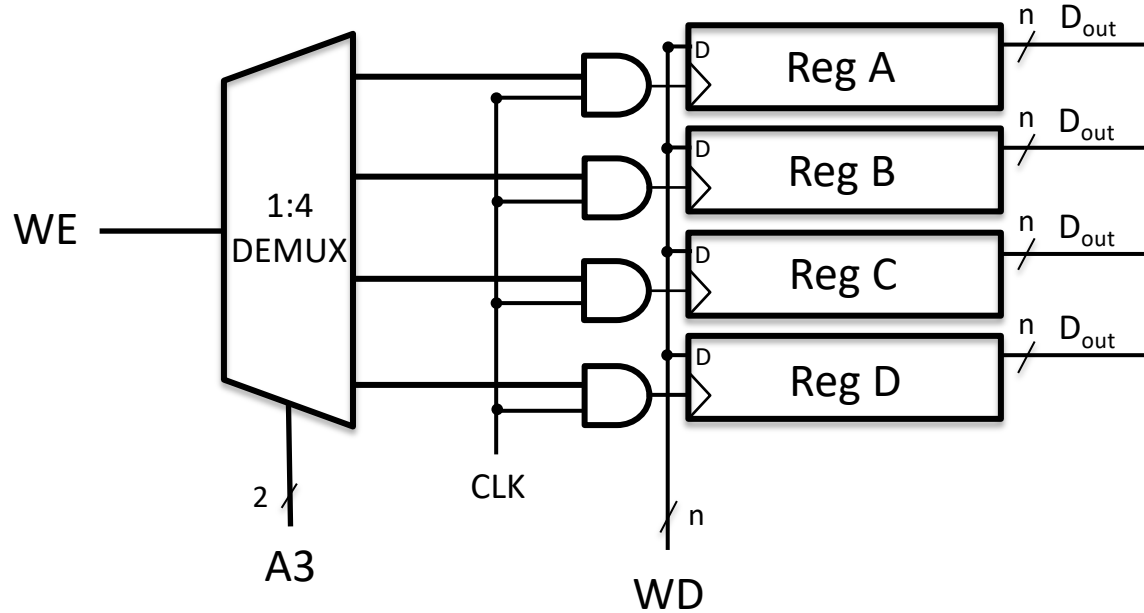

TIMING DIAGRAM

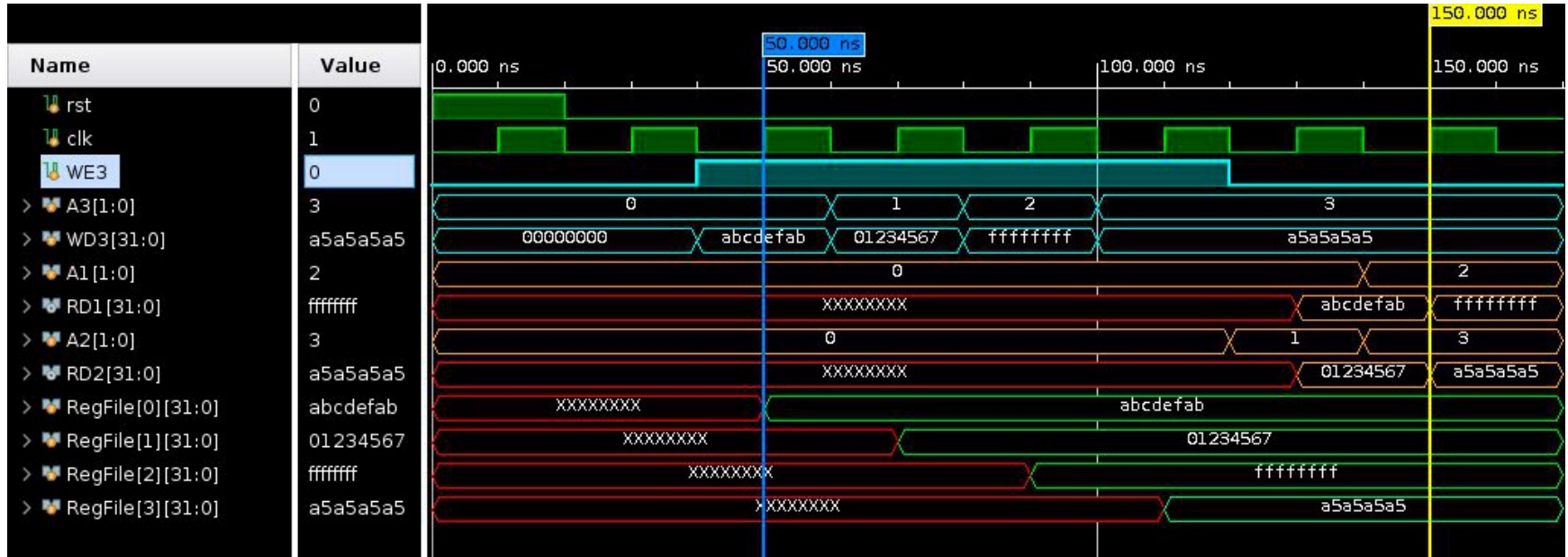


32 32-BIT REGISTER FILE

Simultaneously read from two registers and write into one register


Components:

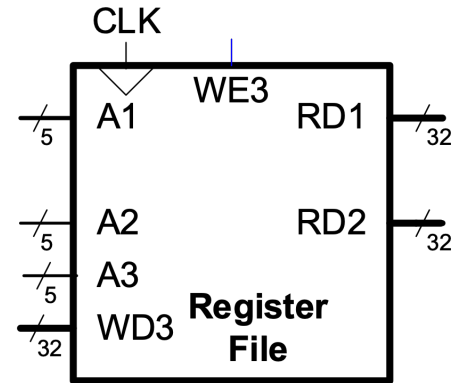1. Multiplexers
2. Registers
3. Demultiplexers



INSTRUCTION MEMORY

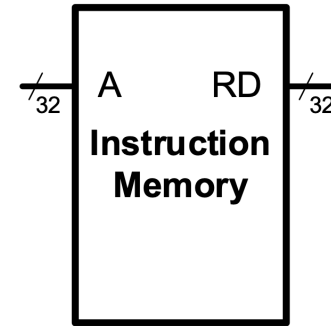
- Stores the program
- Read data (RD) for a given address (A)



For this class, we will assume we cannot write to Instruction Memory.

DATA MEMORY

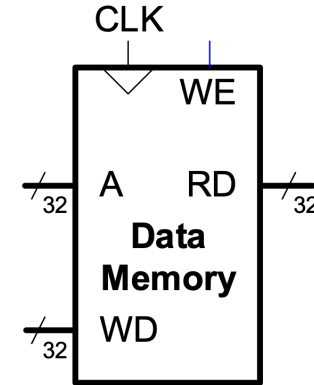- Contains data needed by the program
 - Read data (RD) from a given address (A)
 - Write data (WD) to a given address (A)



IS THIS IT?

- Are the RAMs in your laptop just made of flipflops?
- Are your hard disks in your computer systems just made of flipflops?
- Do you have other memory components in your computer?

MEMORY HIERARCHY

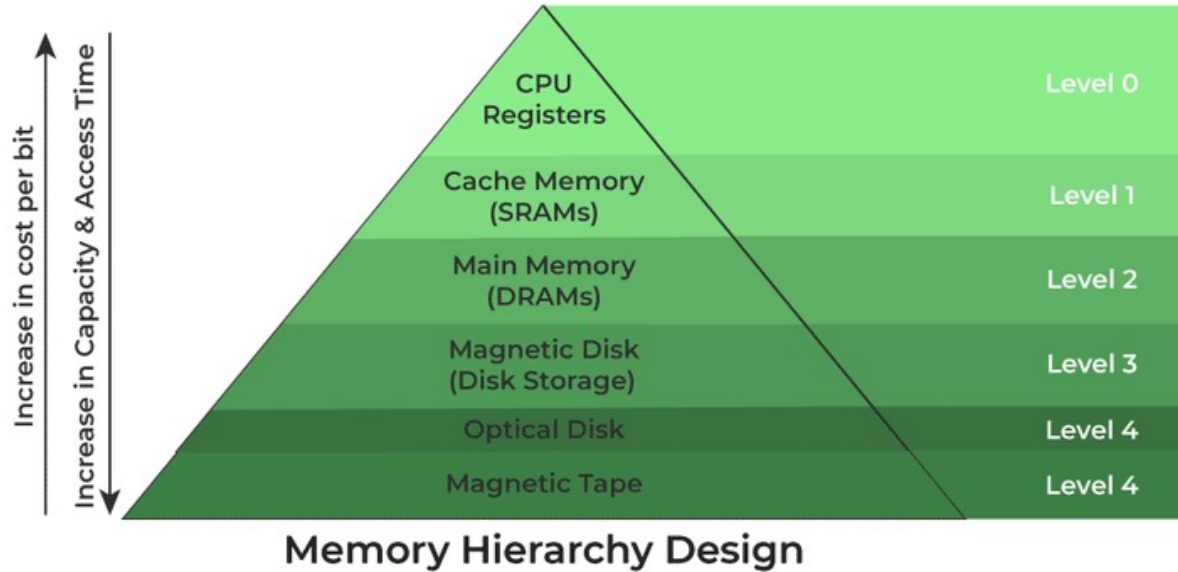



Figure from: <https://www.geeksforgeeks.org/memory-hierarchy-design-and-its-characteristics/>

EXERCISE

What should be the input signals to

1. write 0xABCD to Register #8?
2. read from Register #31 and Register #16?

Register counting starts from 0

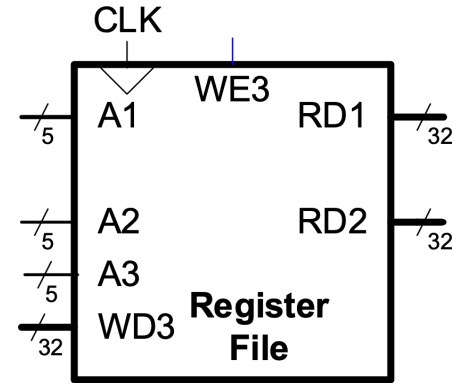

QUESTIONS?

