

# COMPUTER SYSTEMS AND ORGANIZATION

## Adders

---

Daniel Graham




UNIVERSITY  
of VIRGINIA


ENGINEERING

# REVIEW

# THE IDEA

 

# 4-BIT ADDER

 

Great now let's build it with gates.

# ADDING

$$\begin{array}{r} 1\ 1\ 1\ 1 \leftarrow \text{Carries} \\ 0\ 1\ 1\ 1 \\ + 1\ 0\ 1\ 1 \\ \hline 0\ 0\ 1\ 0 \end{array}$$

Let start by building a half adder something that just adds two bits.

Let's build a truth table.

A	B	A + B	C.out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

We can implement  
A + B with an **XOR gate**  
And the C.out (Carry out)  
With an **AND gate**

# ADDING


$$\begin{array}{r} 1\ 1\ 1\ 1 \leftarrow \text{Carries} \\ 0\ 1\ 1\ 1 \\ + 1\ 0\ 1\ 1 \\ \hline 0\ 0\ 1\ 0 \end{array}$$

Let start by building a half adder  
something that just adds two bits.


Let's build a truth table.

A	B	A + B	C.out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 We can implement  
A + B with an **XOR gate**  
And the C.out (Carry out)  
With an **AND gate**



# HALF ADDER DEMO

 


<https://tinyurl.com/ygpea8v4>

<http://www.falstad.com/circuit/circuitjs.html?ctz=CQAgjCAMB0l3BWc0FwCwCY0HYEA4cEMEIURTJyBTAWjDACgwE0QMs21KBmANj06VKGKOSZI2rMGI Z8B01sNEIGAGXAZ5vSnkphtbUQDMAhgBsAzlXJQ1GgZJC62HEZVOXrSSAwDu9lykDRx9-fWE0cIDQ8AMwTUDov1il1kcQ5PitPQBOESiYsDyU8GLiXlswsoQK9JrK0vzgyIMfAFkQOXAZEDR9brS2FAYOrqxKPtquQwxhoA>

 
# ADDING

1 1 1 1 ← Carries  
0 1 1 1  
+ 1 0 1 1  
-----  
0 0 1 0

We can implement  
 $A + B$  with an **XOR gate**  
And the C.out (Carry out)  
With an **AND gate**



## Half Adder

 


A	B	C <sub>out</sub>	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$
$$C_{out} = AB$$



## Half Adder

 


A	B	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

## Full Adder

 


$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

$$\begin{array}{r}
 1\ 1\ 1\ 1 \quad \leftarrow \text{Carries} \\
 0\ 1\ 1\ 1 \\
 + 1\ 0\ 1\ 1 \\
 \hline
 0\ 0\ 1\ 0
 \end{array}$$

# Full Adder

 


$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$
 
$$\begin{array}{r} 1\ 1\ 1\ 1 \\ 0\ 1\ 1\ 1 \\ +\ 1\ 0\ 1\ 1 \\ \hline 0\ 0\ 1\ 0 \end{array} \quad \leftarrow \text{Carries}$$




C.out has been rewritten to reduce the number of gates needed.
 
# DEMO FULL ADDER


<https://tinyurl.com/2cfbbshs>

<http://www.falstad.com/circuit/circuitjs.html?ctz=CQAgjCAMB0l3BWc0FwCwCY0HYEA4cEMEIURTJyBTAWjDACgwE1w1WNsMRPveoeAhExYgAzGIBsPBNLSSOsgd1lMA7jy6buYyBy2R14vdvFTThjROlhJlfrqWz0rPa1uoR-p59YvGn6sYOW8-s4OdqYY4d54eOAYCfLBSV4AsuQAnNyOIJL+eXwoRvR88WwcFc4hwWDceJRIASCN4PWt9krObcQ2oX1eADKdMnIJg7kgAGYAhgA2AM5U5MPt5ckTFVNzSytIhiO1YaxoE-47C8urNaHHzcc1HfcdSQnOKYnJCpUt1uA5YzBQH OXTAnQmfgfH6DBDYVzdlxwhHSZE8SDvBiZNEYDH5C544rCZhNO5pN5fZSrYlKf5geEgT706T2lQibhMqlIQF5VmqlA>



# RIPPLE CARRY ADDER


Next let's build a full adder

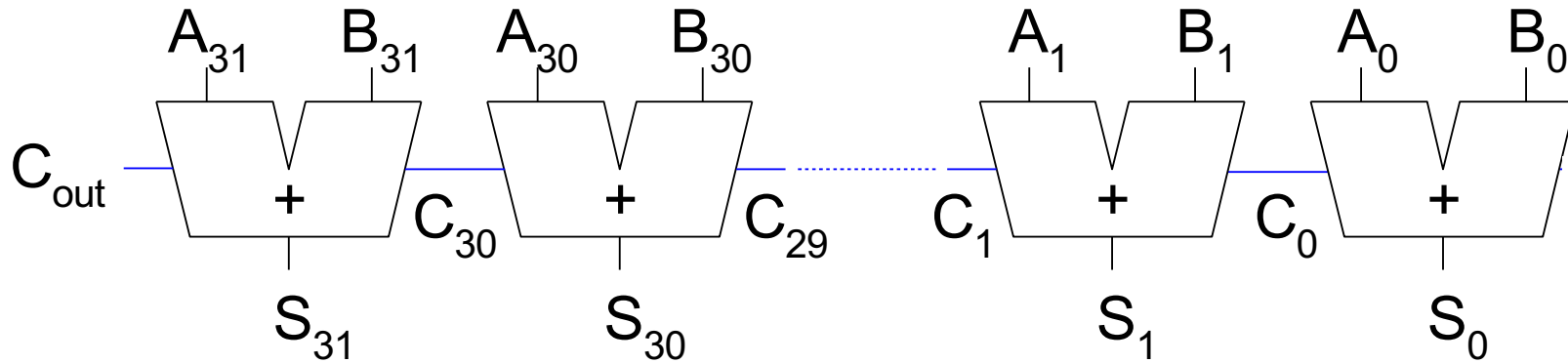

# RIPPLE CARRY ADDER

1 1 1 1 ← Carries

0 1 1 1  
+ 1 0 1 1  
-----  
1 1 1 0

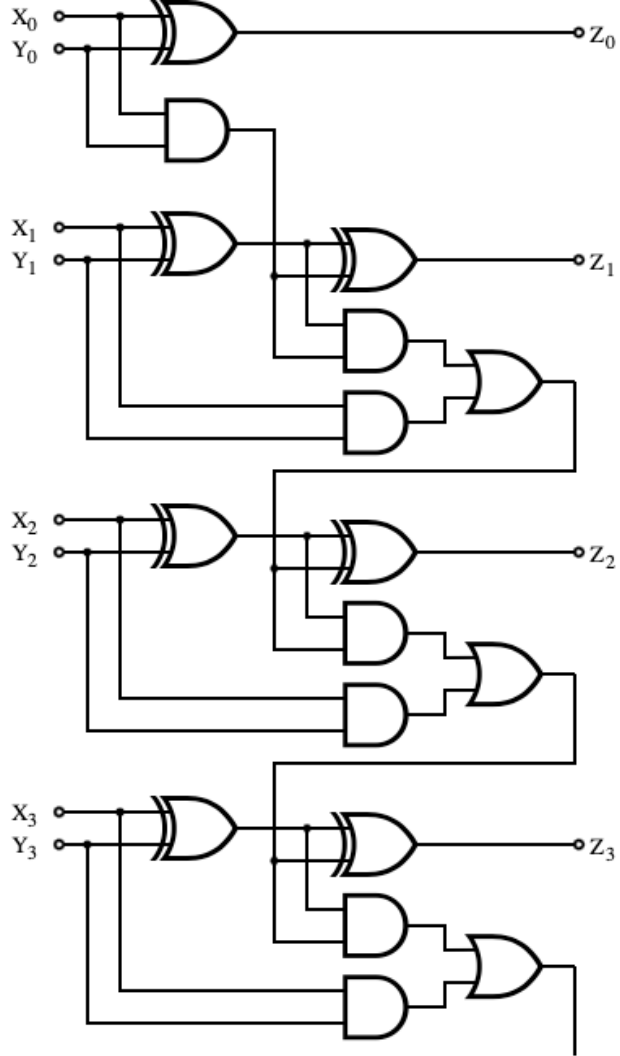



# ***Contents***


1. Clocks
2. Latches
3. Flip Flops

# CLOCKS

A clock is something that produces a periodic signal

Period is length of time for one clock cycle

Example

 


# CLOCKS

Clock frequency Intel Core i-9 3.0GHz

Frequency =  $1 / \text{period}$

Period =  $1 / \text{frequency}$

 




# CLOCKS

Clock frequency Intel Core i-9


3.0GHz. =  $3 \times 10^9 = 3,000,000,000$  cycles per second

Thank is fast.

 


# CLOCKS EDGES

Rising Edge (Also called positive edge)

 

# CLOCKS EDGES


Falling Edge.

 

We will build a single cycle machine it will complete all the computation in a single cycle
 
# USING RING OSCILLATORS TO GENERATE CLOCKS

A clock is something that produces a periodic signal



Let's walk through an example and assume that Q starts off as 0. Draw wave form that results.

$$\text{Frequency} = 1/(2 \cdot t \cdot n)$$


Where  $t$  is time delay of an inverter and  $n$  is number of inverters

# THE D FLIP FLOP


# STORING SINGLE

## Goal

 1. Understand the behavior of a positive edge-triggered D flip-flop.
  - How do we store a bit
  - What happens when the clock changes
  - What does it mean to be a positive edge triggered flip flop
  - What is Q and  $\overline{Q}$



# BUILT SIMULATOR VERSION

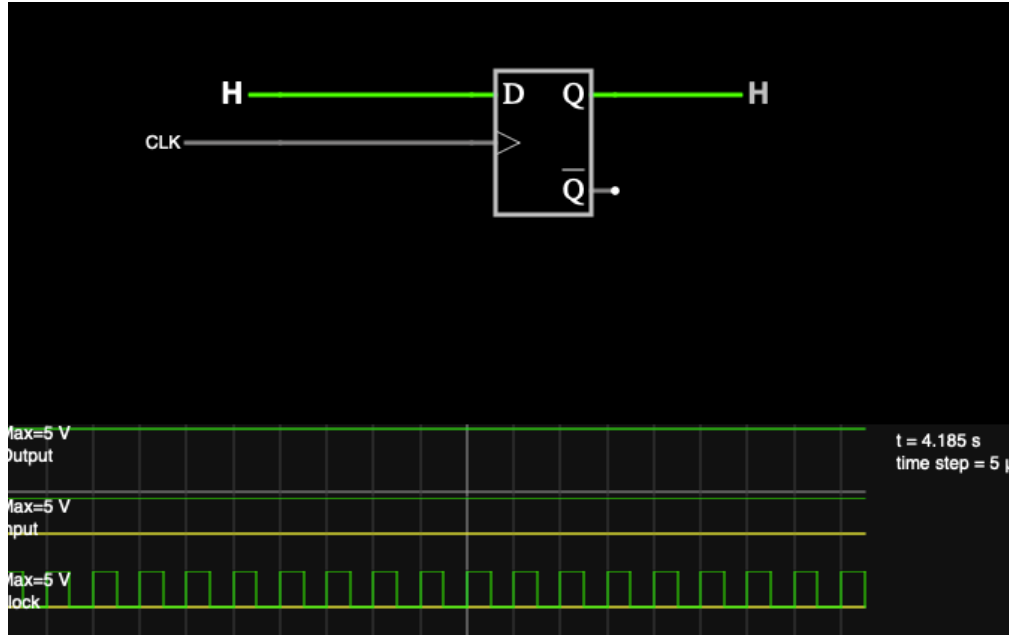

Use this link to experiment with the flipflop during lecture. Try different things as see how it works

<https://tinyurl.com/2dhk5kvg>

<http://www.falstad.com/circuit/circuitjs.html?ctz=CQAgjCAMB0l3BWcMBMcUHYMGZIA4UA2ATmIxAUgoqoQFMBaMMAKDASUPxABZsUQGPD178oFFgHcQXPKIE88VPgMhSZ3HoRGLI2qCwAyyJfN6KzVCADMAhgBsAznWpqASib064vfRAFgPijQSMFIVDAILACygpA6YkrKYIRhLAD21PrKkKSu0BBWIADyAK4ALgAOFrNgMil5eeGw8GSECIQo4SABINggAJYAdtXltQLZvLnE+fC5GO2d3QIC-QDG9ulrANYsQA>

# D FLIP FLOP

Two inputs and Two outputs

## Inputs


D – Data in (The single bit that we want the flip flop to store)

Clock – the output wave from the clocks we discussed earlier

## Output

Q – The value of the internal state. 1 if the internal state is one and zero if the internal state is 0

Q (bar) – Is the inverse of Q.

 




# STATE OF A D FLIP-FLOP

Let assume that the D flip state is where its internal state is zero


What is the value of Q and Q bar?

 
 
# SETTING A D FLIP-FLOP TO 1


Now let's set the internal state of the Flip-Flop to 1 by setting D to 1

Notice that the outputs Q and Q (bar) also change.


 
# SETTING A D FLIP-FLOP TO 0


We can set the flip back to zero by setting D to **0**.  
Notice that Q is now 0 and Q (bar) is now 1.





# WHAT ABOUT THE CLOCK

The Clock determines timing. Specifically

 1. When the values change
2. How long the values remain. Let's look at an example. Where goes from 0 to 1





# WHAT ABOUT THE CLOCK

  



Notice that Q doesn't change until the rising edge

# WHAT ABOUT THE CLOCK

  

Notice that Q doesn't change until the rising edge
  
# THE FLIP FLOP HOLD HOLDS THE VALUE FOR A CLOCK CYCLE



# BUILDING A REGISTER FROM FLIP FLOPS



# BUILDING A REGISTER FROM FLIP FLOPS

What is a register?


Is a memory unit that stores bit for 1 or more or more clock cycles

Who could we build a 3-bit register?

Examples of things we can store in a register


The number 5 in binary 101 (This would need a three-bit register)

# BUILDING A REGISTER FROM FLIP FLOPS

 

Who could we build a 3-bit register? We can build a 3 bit register with three flip-flops

# BUILDING A REGISTER FROM FLIP FLOPS

 

Removed Q (bar) for reability

# REGISTER SYMBOLS




# 3-BIT COUNTER


Let's put it all together and build a 3-bit counter

Circuit that counts from

 000,  
001,  
010,  
011,  
100,  
101,  
110,  
111


 
# DRAWING 3-BIT COUNTER OVER SEVERAL CYCLES



Draw the Timing Diagram

# EXAM QUESTIONS SPRING 2023

11. [4 points] The register that we discussed in class (the positive-edge-triggered D flip-flop) has inputs `D` and `clock` and output `Q`. If `Q` is 1 and the `clock` is transitioning from 1 to 0, which of the following is true? *Fill in the circle completely for all that apply.*
- ☐ `D` must also be 1 (not 0)
  - ☐ `D` may be 0 or 1
  - ☐ `Q` will transition from 1 to 0 with the clock
  - ☐ `Q` will transition to the value of `D` when the clock transitions to 0
12. [4 points] To build a 4-bit counter circuit, we could directly connect the outputs of the circuit back to the inputs without the need of a register.
- ☐ True
  - ☐ False

11. [4 points] The register that we discussed in class (the positive-edge-triggered D flip-flop) has inputs `D` and `clock` and output `Q`. If `Q` is 1 and the `clock` is transitioning from 1 to 0, which of the following is true? *Fill in the circle completely for all that apply.*
- ☐ `D` must also be 1 (not 0)
  - ☐ `D` may be 0 or 1
  - ☐ `Q` will transition from 1 to 0 with the clock
  - ☐ `Q` will transition to the value of `D` when the clock transitions to 0

**B**


12. [4 points] To build a 4-bit counter circuit, we could directly connect the outputs of the circuit back to the inputs without the need of a register.
- ☐ True
  - ☐ False

**False**



**Page 5: Circuits**

 10. [16 points] In class, we discussed a 4-bit increment circuit below that added 1 to the input.



How can we change this circuit to instead increment by 2, i.e.,  $x += 2$ ? Draw the new circuit below. *Note: you should not use more gates than the original circuit.*

