

# CS0 2130

## TOY Processor

---

Daniel G. Graham PhD



UNIVERSITY  
of VIRGINIA

ENGINEERING



1. A full overview of Toy ISA
2. Build a machine (Toy Processor) that can execute our Toy ISA
3. Discuss the fetch, decode, execute, memory, and writeback stages
4. Discuss the steps need to synthesize or toy processor

icode	b	meaning
0		<b>rA = rB</b>
1		<b>rA += rB</b>
2		<b>rA &amp;= rB</b>
3		<b>rA = read from memory at address rB</b>
4		<b>write rA to memory at address rB</b>
5	0	<b>rA = ~rA</b>
	1	<b>rA = -rA</b>
	2	<b>rA = !rA</b>
	3	<b>rA = pc</b>
6	0	<b>rA = read from memory at pc + 1</b>
	1	<b>rA += read from memory at pc + 1</b>
	2	<b>rA &amp;= read from memory at pc + 1</b>
	3	<b>rA = read from memory at the address stored at pc + 1</b>
		For icode 6, increase <b>pc</b> by 2 at end of instruction
7		Compare <b>rA</b> as 8-bit 2's-complement to <b>0</b> if <b>rA &lt;= 0</b> set <b>pc = rB</b> else increment <b>pc</b> as normal

## FULL ISA

Let look at each  
of these  
instructions


# EXAM QUESTION

9. [8 points] Complete the table below listing all the register values as hex digits after the following code executes. Assume that all registers start with value 0x00.

6c 20 60 ff 2c 04 54 19

Register	Value
0	
1	
2	
3	

icode	b	meaning
0		<b>rA</b> = <b>rB</b>
1		<b>rA</b> += <b>rB</b>
2		<b>rA</b> &= <b>rB</b>
3		<b>rA</b> = read from memory at address <b>rB</b>
4		write <b>rA</b> to memory at address <b>rB</b>
5	0	<b>rA</b> = ~ <b>rA</b>
	1	<b>rA</b> = - <b>rA</b>
	2	<b>rA</b> = ! <b>rA</b>
	3	<b>rA</b> = <b>pc</b>
6	0	<b>rA</b> = read from memory at <b>pc</b> + 1
	1	<b>rA</b> += read from memory at <b>pc</b> + 1
	2	<b>rA</b> &= read from memory at <b>pc</b> + 1
	3	<b>rA</b> = read from memory at the address stored at <b>pc</b> + 1 For icode 6, increase <b>pc</b> by 2 at end of instruction
7		Compare <b>rA</b> as 8-bit 2's-complement to 0 if <b>rA</b> <= 0 set <b>pc</b> = <b>rB</b> else increment <b>pc</b> as normal

 

6c 20 60 FF 2c 04 54 19

Register	Value
0	
1	
2	
3	

# EXAM QUESTION



9. [8 points] Complete the table below listing all the register values as hex digits after the following code executes. Assume that all registers start with value 0x00.

6c 20 60 FF 2c 04 54 19

Register	Value
0	09
1	07
2	00
3	2D

# LET'S BUILD A TOY PROCESSOR THAT CAN EXECUTE OUR TOY ISA
  
# INSTRUCTION MEMORY AND INSTRUCTION REGISTER




Instruction register (IR)

Our diagram is going to have several comments so I will not draw the IR

Note: input and output widths on the Instruction memory. The memory is byte-addressable but reads 2 bytes at a time



# 1 BYTE AND 2 BYTE INSTRUCTIONS

 


We'll add a mux that will select passing one to adder or two.

The mux will be controlled with a control line  $C_0$ . But what component provides the control signal? Answer the Controller



# HARDWIRED CONTROL UNIT

icode	b	$C_0$	....	$C_n$
6	x	1		
....				

 

icode	b	meaning
0		<b>rA = rB</b>
1		<b>rA += rB</b>
2		<b>rA &amp;= rB</b>
3		<b>rA = read from memory at address rB</b>
4		<b>write rA to memory at address rB</b>
5	0	<b>rA = ~rA</b>
	1	<b>rA = -rA</b>
	2	<b>rA = !rA</b>
	3	<b>rA = pc</b>
6	0	<b>rA = read from memory at pc + 1</b>
	1	<b>rA += read from memory at pc + 1</b>
	2	<b>rA &amp;= read from memory at pc + 1</b>
	3	<b>rA = read from memory at the address stored at pc + 1</b>
		For icode 6, increase <b>pc</b> by 2 at end of instruction
7		Compare <b>rA</b> as 8-bit 2's-complement to <b>0</b> if <b>rA &lt;= 0</b> set <b>pc = rB</b> else increment <b>pc</b> as normal

icode	b	meaning
0		$rA = rB$
1		$rA += rB$
2		$rA \&= rB$

  


Only the relevant part  
instruction is going to  
register file input.  
Icode section and RB will  
also go to the controller.

These are not depicted for  
simplicity


icode	b	meaning
0		$rA = rB$
1		$rA += rB$
2		$rA \&= rB$

How would we wire up the ALU?

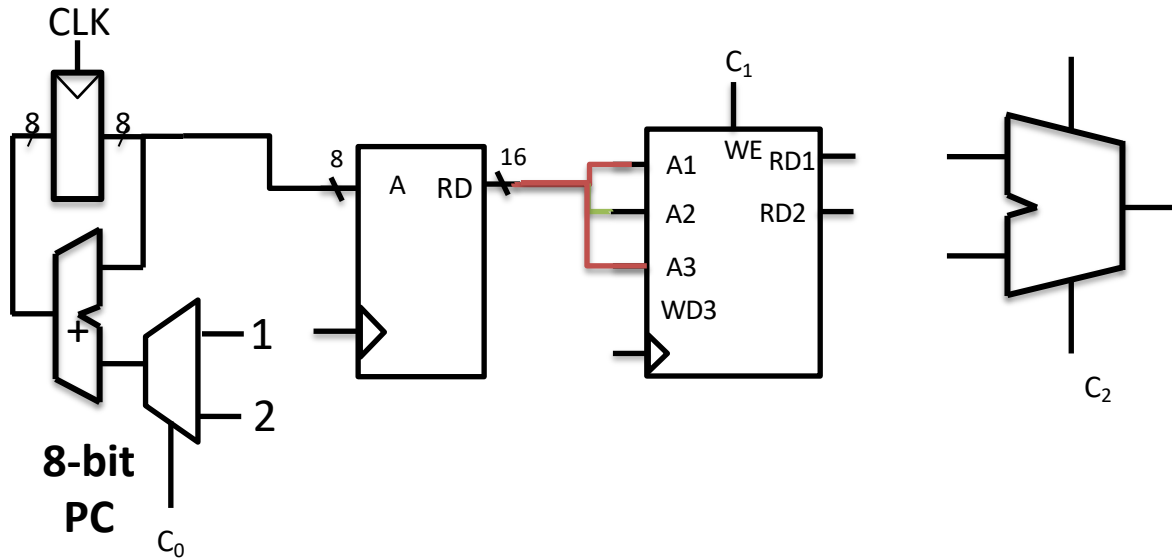

icode	b	meaning
0		$rA = rB$
1		$rA += rB$
2		$rA \&= rB$


Let's run three instructions

 

R	icode	RA	RB
0	000	00	10
0	001	10	10
0	010	10	11

icode	b	meaning
0		$rA = rB$
1		$rA += rB$
2		$rA \&= rB$

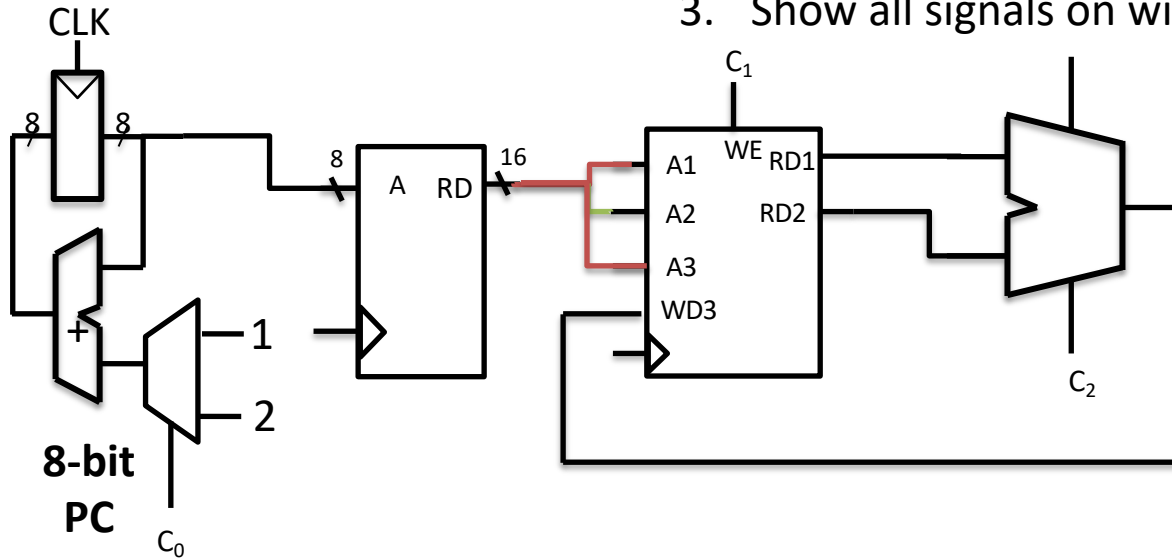
1. Hex encode each instruction
2. Assume  $R0 = 1$ ,  $R1 = 4$ ,  $R2 = 3$ ,  $R3 = 0$
3. Show all signals on wires



R	icode	RA	RB
0	000	00	10
0	001	10	10
0	010	10	11

icode	b	meaning
0		$rA = rB$
1		$rA += rB$
2		$rA \&= rB$

 1. Hex encode each instruction
2. **Assume R0 = 1, R1 = 4, R2 = 3, R3 = 0**
3. Show all signals on wires




R	icode	RA	RB
0	000	00	10
0	001	10	10
0	010	10	11



icode	b	meaning
0		$rA = rB$
1		$rA += rB$
2		$rA \&= rB$

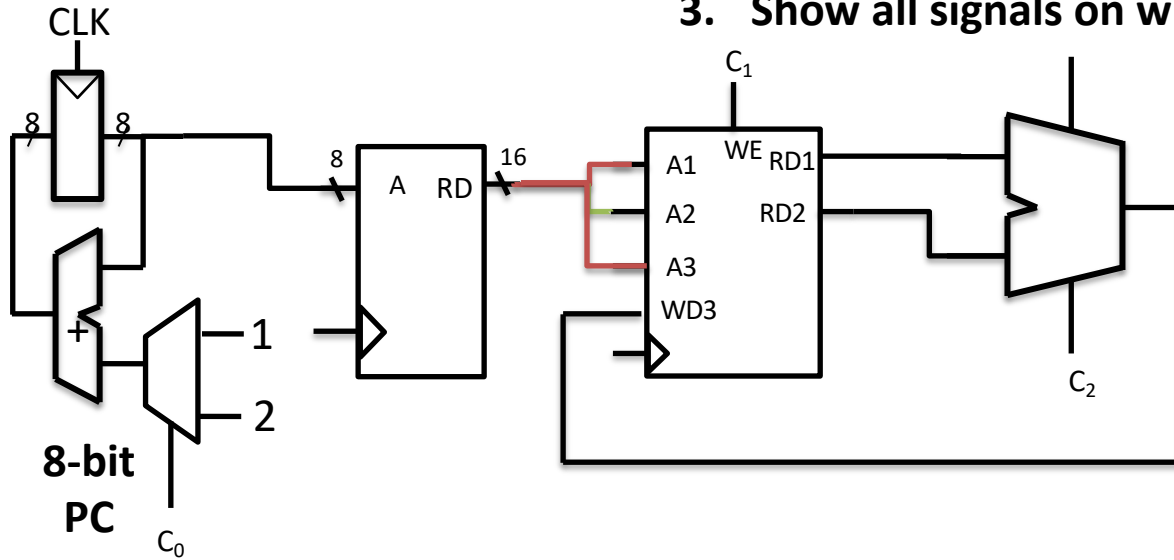1. Hex encode each instruction
2. Assume  $R0 = 1$ ,  $R1 = 4$ ,  $R2 = 3$ ,  $R3 = 0$
3. Show all signals on wires



R	icode	RA	RB
0	000	00	10
0	001	10	10
0	010	10	11

# LET'S NEXT INSTRUCTIONS THAT USE MAIN MEMORY

icode	b	meaning
0		$rA = rB$
1		$rA += rB$
2		$rA \&= rB$
3		$rA = \text{read from memory at address } rB$
4		write $rA$ to memory at address $rB$
5	0	$rA = \sim rA$
	1	$rA = -rA$
	2	$rA = !rA$
	3	$rA = pc$
6	0	$rA = \text{read from memory at } pc + 1$
	1	$rA += \text{read from memory at } pc + 1$
	2	$rA \&= \text{read from memory at } pc + 1$
	3	$rA = \text{read from memory at the address stored at } pc + 1$
		For icode 6, increase $pc$ by 2 at end of instruction
7		Compare $rA$ as 8-bit 2's-complement to 0 if $rA \leq 0$ set $pc = rB$ else increment $pc$ as normal


3

 $rA$  = read from memory at address  $rB$ 

4

write  $rA$  to memory at address  $rB$ 

 
Talk to use neighbor to see if you can wire this up.



3

 $rA$  = read from memory at address  $rB$ 


4

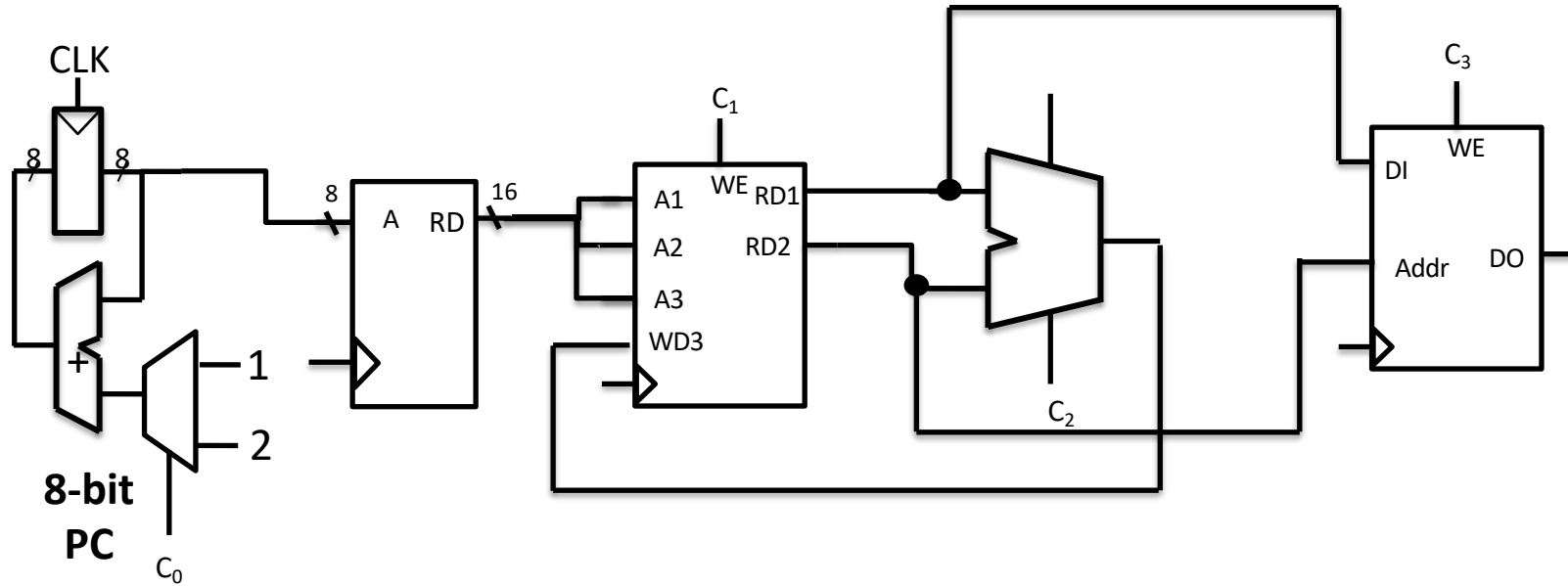write  $rA$  to memory at address  $rB$ 

3

 $rA$  = read from memory at address  $rB$ 

4

 write  $rA$  to memory at address  $rB$ Writing **labels** for a cleaner look


3

**rA = read from memory at address rB**

4

write rA to memory at address rB

 Looks like we have a conflict. Thoughts on how we could fix this?




3

 **$rA$  = read from memory at address  $rB$** 

4

write  $rA$  to memory at address  $rB$ 


Let's execute some sample instructions

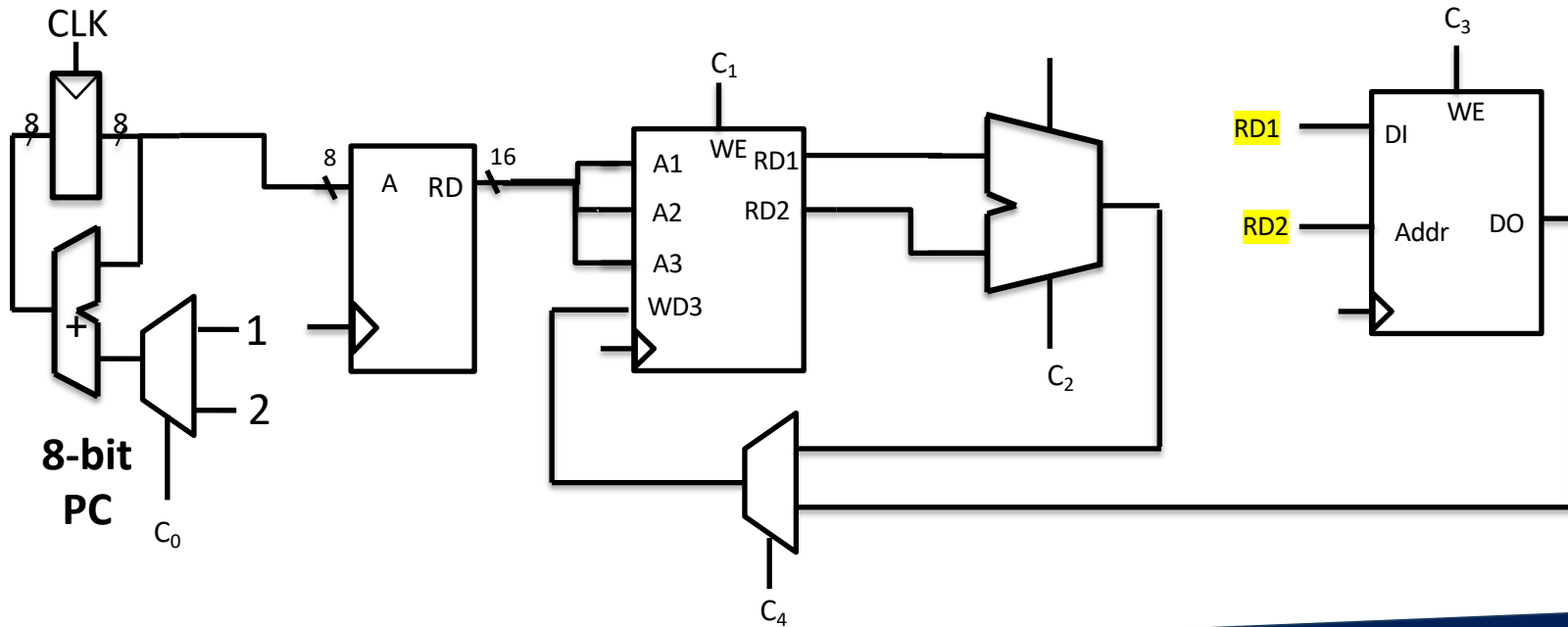



1	$rA += rB$
2	$rA \&= rB$
3	$rA = \text{read from memory at address } rB$
4	$\text{write } rA \text{ to memory at address } rB$

Let's execute some sample instructions

 

# NEXT TIME

icode	b	meaning
0		$rA = rB$
1		$rA += rB$
2		$rA \&= rB$
3		$rA$ = read from memory at address $rB$
4		write $rA$ to memory at address $rB$
5	0	$rA = \sim rA$
	1	$rA = -rA$
	2	$rA = !rA$
	3	$rA = pc$
6	0	$rA$ = read from memory at $pc + 1$
	1	$rA +=$ read from memory at $pc + 1$
	2	$rA \&=$ read from memory at $pc + 1$
	3	$rA$ = read from memory at the address stored at $pc + 1$ For icode 6, increase $pc$ by 2 at end of instruction
7		Compare $rA$ as 8-bit 2's-complement to 0 if $rA \leq 0$ set $pc = rB$ else increment $pc$ as normal

- (d) Throughout the semester we looked at various components associated with a single cycle processor. Here we designed a simple machine that we call the Interceptor 1000. This machine has only two instructions, listed below by their opcodes:

0. **nop** which does nothing

1. **intcep** \$x, \$m, \$b which computes  $mx + b$

An example instruction for this machine might be **intcep 2 3 1** meaning  $x$  is 2,  $m$  is 3 and  $b$  is 1. This instruction would be encoded as follows:

0 1 2 3 4 5 6 7 8 9 a b c d e f

1	0	0	0	1	0	0	0	1	1	0	0	0	0	1
---	---	---	---	---	---	---	---	---	---	---	---	---	---	---

In the diagram below, **O(1)** represents the opcode that is 1 bit long, while **X(5)** represents the  $x$  value that is 5 bits long.

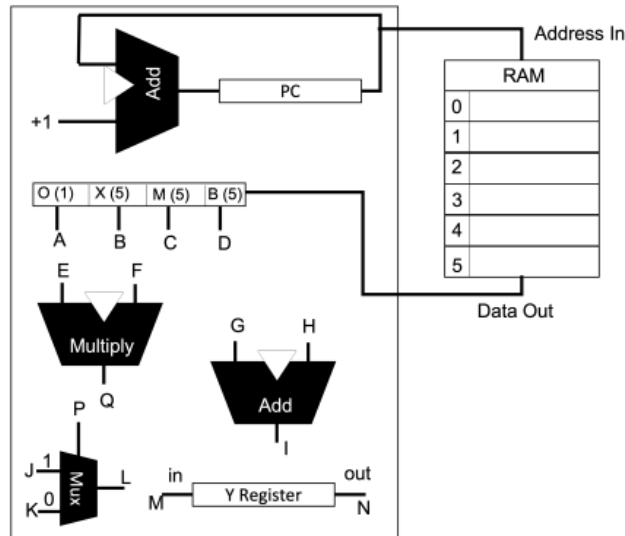


Figure 1: Block Diagram for Interceptor 10000

## EXAM QUESTION

Show how to complete the diagram by writing the name of the wire each given wire should be connected to. For example, if  $A$  is connected to  $E$ , write  $E$  in the box next to  $A$ .


A	→	
B	→	
C	→	
D	→	

I	→	
L	→	
N	→	
Q	→	




5	0	$rA = \sim rA$
	1	$rA = -rA$
	2	$rA = !rA$
3		$rA = pc$

Draw out the flow here

 


5	0	$rA = \sim rA$
1	1	$rA = -rA$
2	2	$rA = !rA$
3	3	$rA = pc$

How can we update RA with the PC value?

 


5	0	$rA = \sim rA$
	1	$rA = -rA$
	2	$rA = !rA$
	3	$rA = pc$

How can we update RA with the PC value?

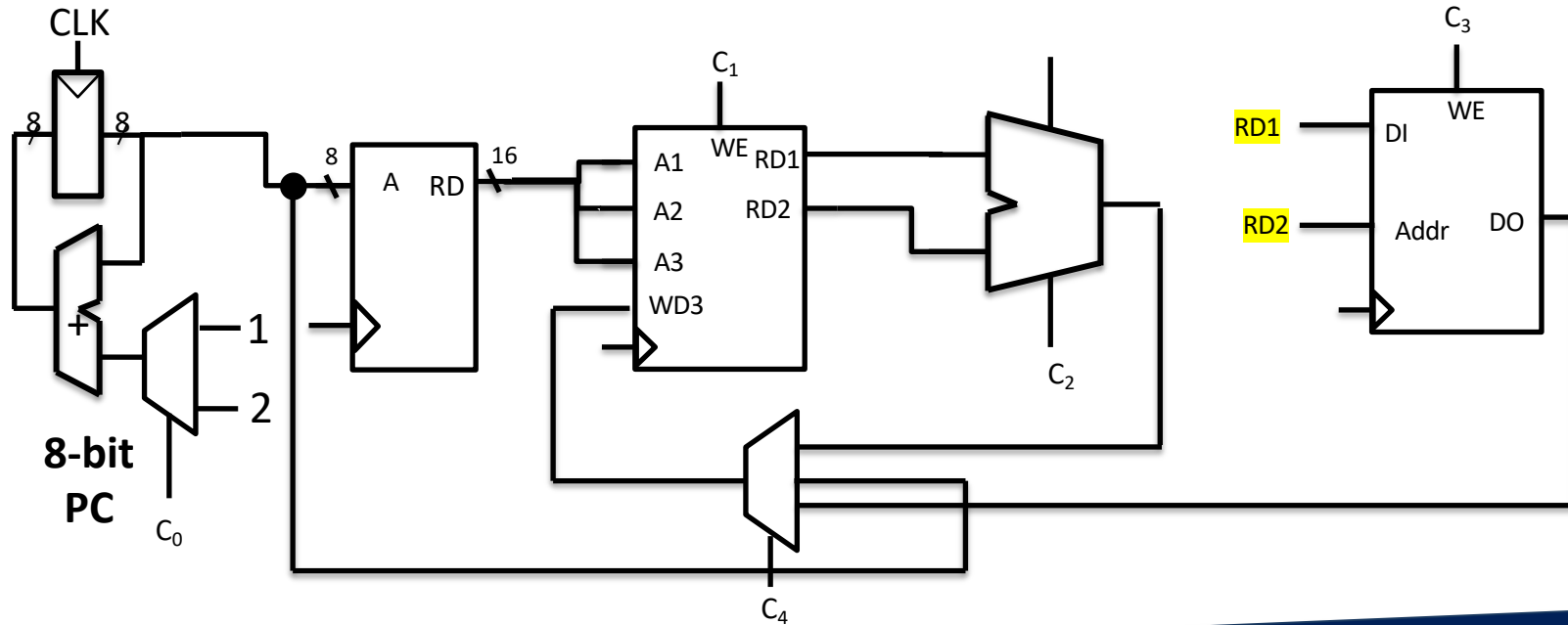

5	0	$rA = \sim rA$
	1	$rA = -rA$
	2	$rA = !rA$
	3	$rA = pc$

Changed it to just be the label

 




6	0	$rA = \text{read from memory at } \boxed{pc + 1}$
1		$rA += \text{read from memory at } pc + 1$
2		$rA \&= \text{read from memory at } pc + 1$
3		$rA = \text{read from memory at the address stored at } pc + 1$

The immediate

immediate

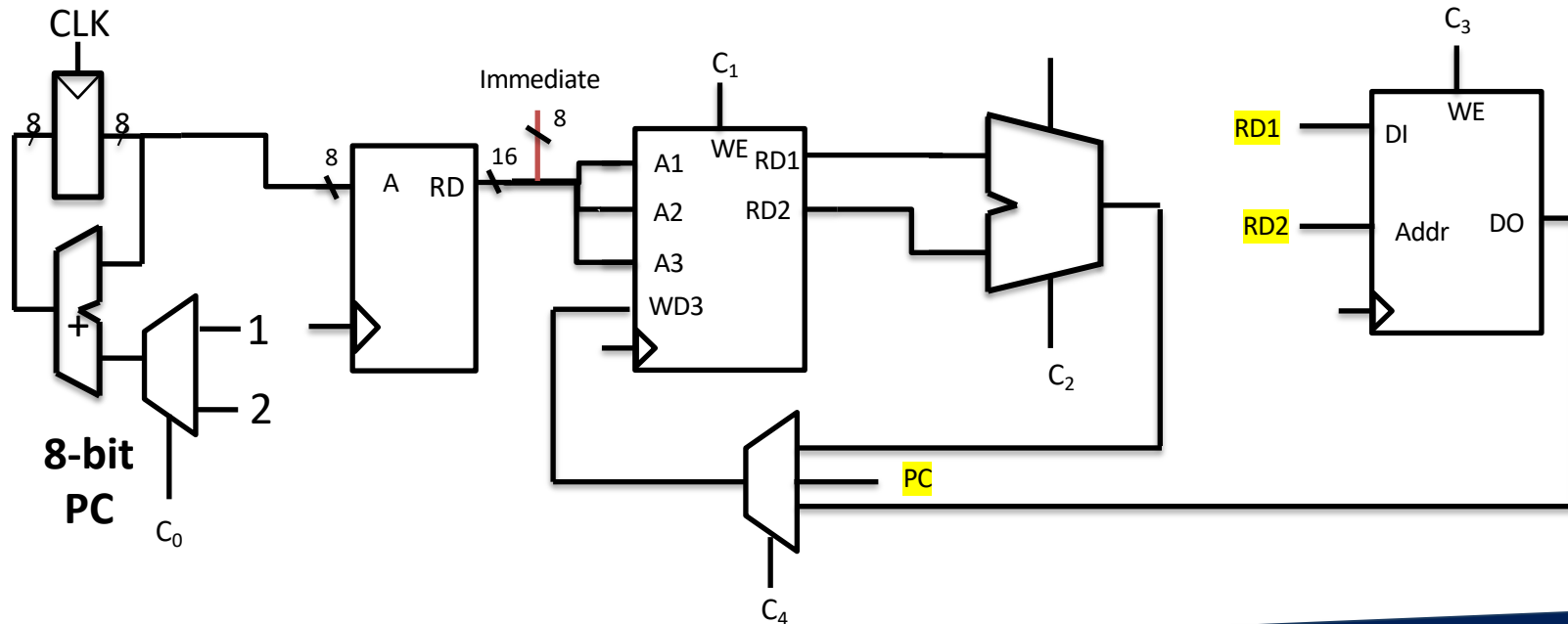




6	0	<b>rA = read from memory at pc + 1</b>
1		rA += read from memory at pc + 1
2		rA &= read from memory at pc + 1
3		rA = read from memory at the address stored at pc + 1

Walk through the flow of an example instruction

R	icode	RA	RB
---	-------	----	----

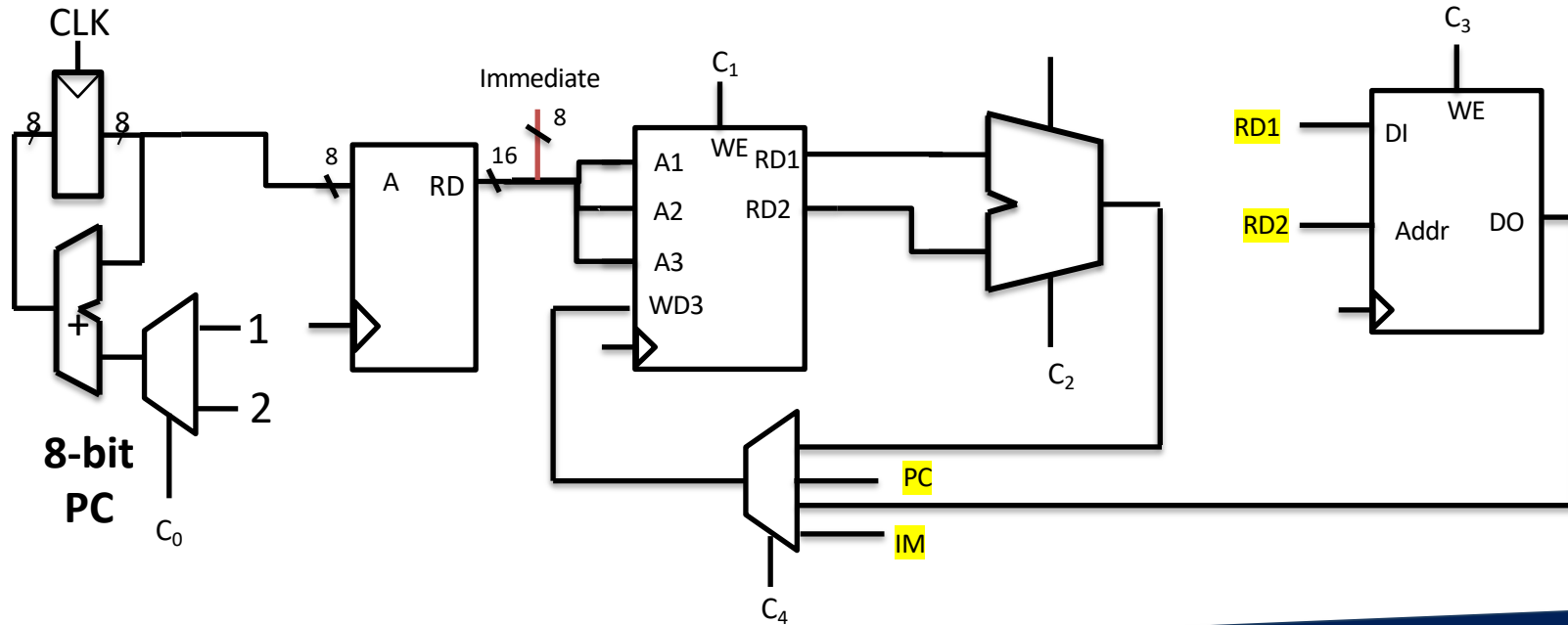




6	0	$rA = \text{read from memory at } pc + 1$
1	1	$rA += \text{read from memory at } pc + 1$
2	2	$rA \&= \text{read from memory at } pc + 1$


Again we just need a mux

3		$rA = \text{read from memory at the address stored at } pc + 1$
---	--	---

 


6	0	$rA = \text{read from memory at } pc + 1$
	1	$rA += \text{read from memory at } pc + 1$
	2	$rA \&= \text{read from memory at } pc + 1$
	3	$rA = \text{read from memory at the address stored at } pc + 1$

What about these instructions

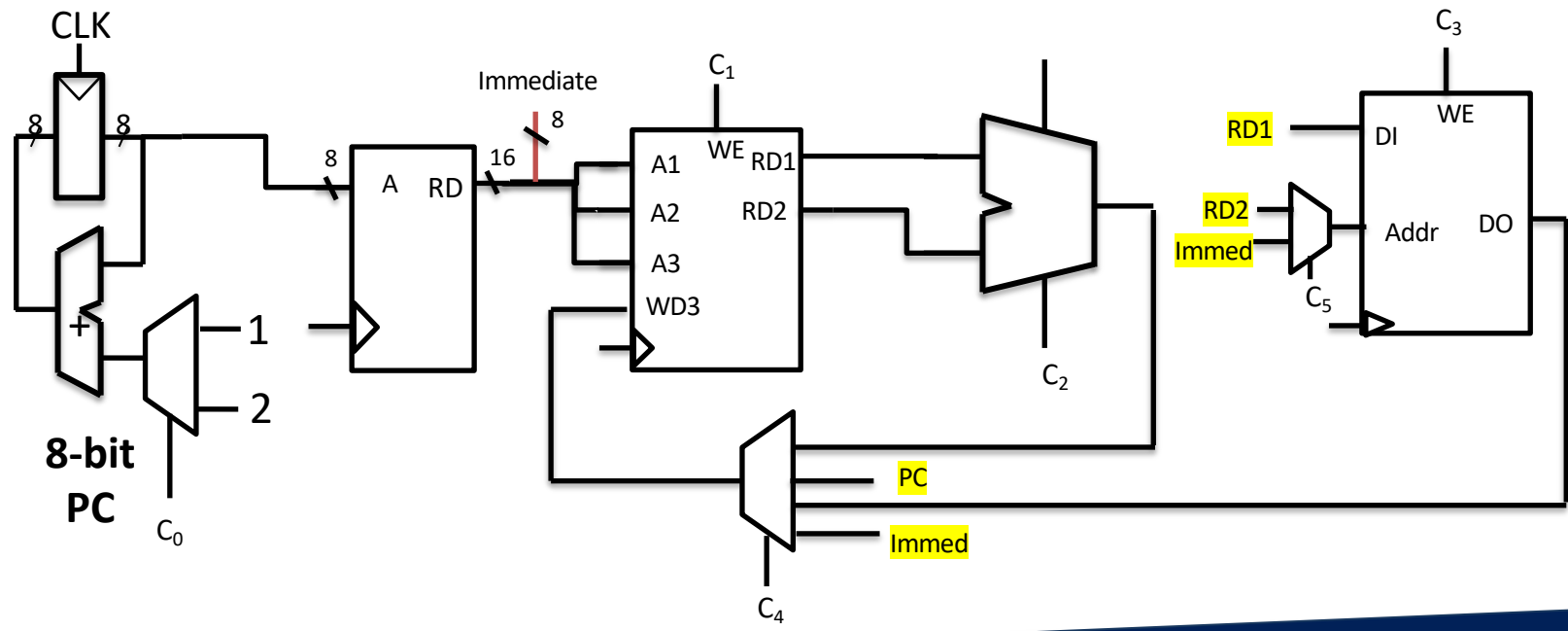

6	0	$rA = \text{read from memory at } pc + 1$
	1	$rA += \text{read from memory at } pc + 1$
	2	$rA \&= \text{read from memory at } pc + 1$
	3	$rA = \text{read from memory at the address stored at } pc + 1$

Just need a mux

 

# NOW FOR OUR FINAL INSTRUCTIONS

## OUR CONDITIONAL JUMP




7

Compare  $rA$  as 8-bit 2's-complement to 0  
 if  $rA \leq 0$  set  $pc = rB$   
 else increment  $pc$  as normal

How do we implement  
 this one?

Talk to your neighbor

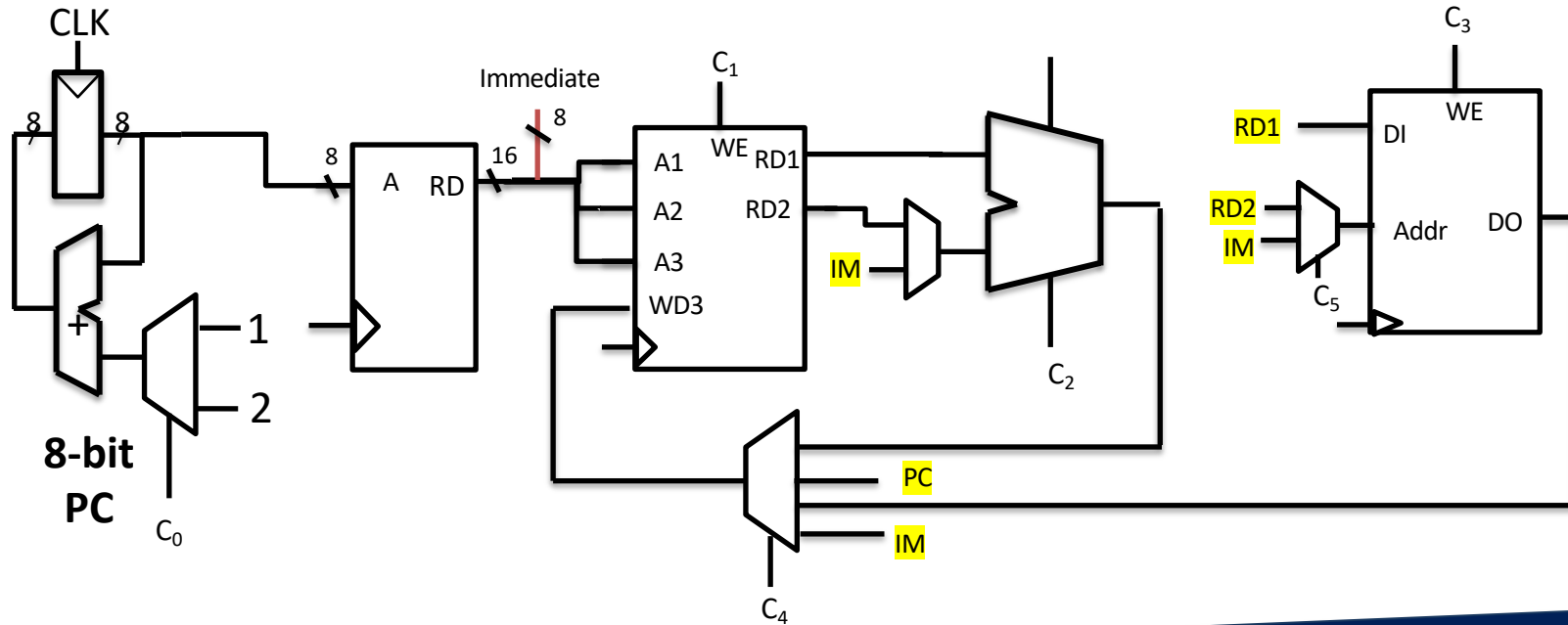


```

Compare rA as 8-bit 2's-complement to 0
if rA <= 0 set pc = rB
else increment pc as normal

```

Notice the sign  
flag output by  
ALU

 


```

Compare rA as 8-bit 2's-complement to 0
if rA <= 0 set pc = rB
else increment pc as normal


```

R	icode	RA	RB
---	-------	----	----

 


# WHAT ABOUT DETAILS OF THE MAIN MEMORY

 1. How is it implemented?
2. How does it work underhood?
3. Don't worry we'll answer this in CSO 2.
  1. It is actually a complex hierarchy including a controller, caches, and Hardware support for virtual memory like TLBS (translation lookaside buffers)
  2. It doesn't always return a value in a single cycle so the controller might have to insert nops in the pipeline etc.




# THE MAP (THE MACHINE)

 

<https://github.com/MKrekker/SINGLE-CYCLE-RISC-V>


# RISC-V MACHINE

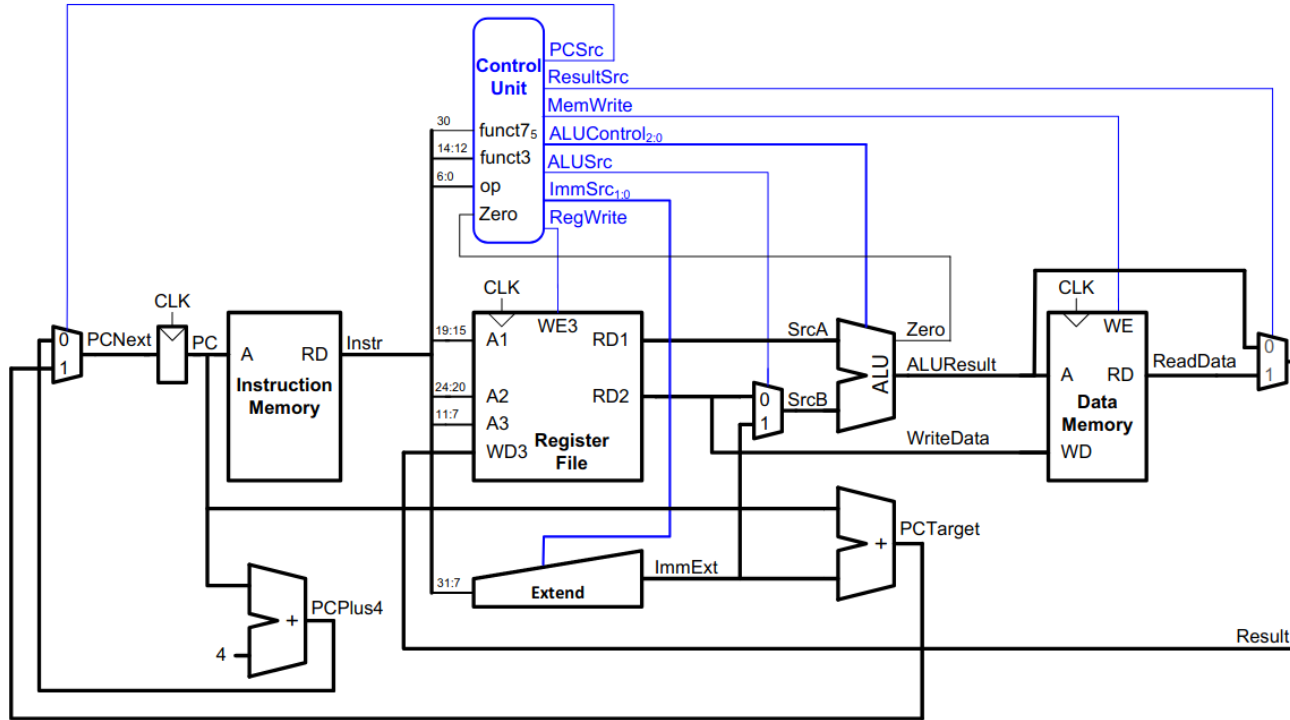

# RISC-V MACHINE

CORE INSTRUCTION FORMATS

	31	27	26	25	24	20	19	15	14	12	11	7	6	0
R	funct7				rs2		rs1		funct3		rd		opcode	
I	imm[11:0]						rs1		funct3		rd		opcode	
S	imm[11:5]				rs2		rs1		funct3		imm[4:0]		opcode	
SB	imm[12 10:5]				rs2		rs1		funct3		imm[4:1 11]		opcode	
U	imm[31:12]										rd		opcode	
UJ	imm[20 10:1 11 19:12]										rd		opcode	

 

# THE ISA ALSO INCLUDES FLOATING LAYOUT SUPPORTED AND REGISTER AND THEIR DESCRIPTION

[https://www.elsevier.com/\\_data/assets/pdf\\_file/0011/297533/RISC-V-Reference-Data.pdf](https://www.elsevier.com/_data/assets/pdf_file/0011/297533/RISC-V-Reference-Data.pdf)

Let's look at the section that describes floating point  
And instruction encodings. Focus many on the  
second page



# THE MAP (THE CODE)

```
#include <stdio.h>
int main() {
    printf("Hello, World!");
    return 0;
}
```



```
0000000000001149 <main>:
    1149: f3 0f 1e fa      endbr64
    114d: 55              push    %rbp
    114e: 48 89 e5        mov     %rsp,%rbp
    1151: 48 8d 05 ac 0e 00 00
    lea    0xeac(%rip),%rax      # 2004
    <_IO_stdin_used+0x4>
    1158: 48 89 c7        mov     %rax,%rdi
    115b: e8 f0 fe ff ff  call    1050 <puts@plt>
    1160: b8 00 00 00 00  mov     $0x0,%eax
    1165: 5d              pop     %rbp
    1166: c3              ret
```

We will not cover this conversion in detail. CS 4620 - Compilers is a class dedicated to building and understanding the program designed to do this conversion.

We'll focus on understanding the output of the program and how this output gets executed on a machine

# NEXT WE'LL TALK ABOUT WRITING PROGRAMS THAT SIMULATE OUR ARCHITECTURE



