

COMPUTER SYSTEMS AND ORGANIZATION

Part 1

Daniel G. Graham Ph.D



UNIVERSITY
of VIRGINIA


ENGINEERING



1. Transistor Fundamentals
2. Build Gates from transistors
3. Using a breadboard to build a gate
4. Combine Gates to build logic circuits
5. Express logic circuits as equations

SKILLS

 1. By the end lecture, you should be able to look at the circuit on the right and tell what it will output given different inputs
2. You should be able to express the circuit as a Boolean logic equation
3. Understand how to combine gates to implement a Boolean logic equation.
4. Combine transistors to implement a gate or logic circuit.




RESOURCES

dbooks.org

Beej's Guide to C Programming


Brian "Beej Jorgensen" Hall

 Beej's Guide to Network Programming Using Internet Sockets




Brian "Beej Jorgensen" Hall

 THIRD EDITION COMPUTER SYSTEMS A PROGRAMMER'S PERSPECTIVE







 


BRYANT • O'HALLARON

Digital Design and Computer Architecture RISC-V Edition



MK
MORGAN KAUFMANN

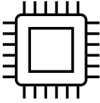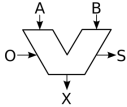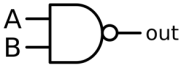Sarah L Harris
David Harris

Application Software	
Operating system	
Architecture	
Micro Architecture	
Gates	
Devices	
Physics	

C

Linux

Risc-V




Data path, Stages

Nand, NOR, NOT ..

PNP NPN Transistors


Electrons

TRANSISTOR

   


THIS WERE WE'LL START OUR JOURNEY

 - **Metal oxide silicon (MOS) transistors:**
 - Polysilicon (used to be **metal**) gate
 - **Oxide** (silicon dioxide) insulator
 - Doped **silicon**




DOPED SILICON

 
- Pure silicon is a poor conductor (no free charges)
- Doped silicon is a good conductor (free charges)
 - n-type (free **n**egative charges, electrons)
 - p-type (free **p**ositive charges, holes)



Silicon Lattice

 


n-Type

 

p-Type


Gate = 0

 OFF (no connection between source and drain)




Gate = 1

ON (channel between source and drain)

 


THINKING OF TRANSISTORS AS SWITCHES


nMOS

 

$g = 0$

 

$g = 1$

 

CAN WE USER TRANSISTORS TO BUILD GATES


Questions we need to answer

- What are logic gates?
- How do logic gates work?
- Are there different types of gates?

WHAT ARE LOGIC GATES

- Logic gates are circuits that perform logic functions
 - such as AND, OR, (NOT) , etc
- Logic gates have different symbols and their behavior is normally described using a truth table.
-


AND

 

$$Y = AB$$


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

BUILD AN AND GATE FROM TRANSISTORS

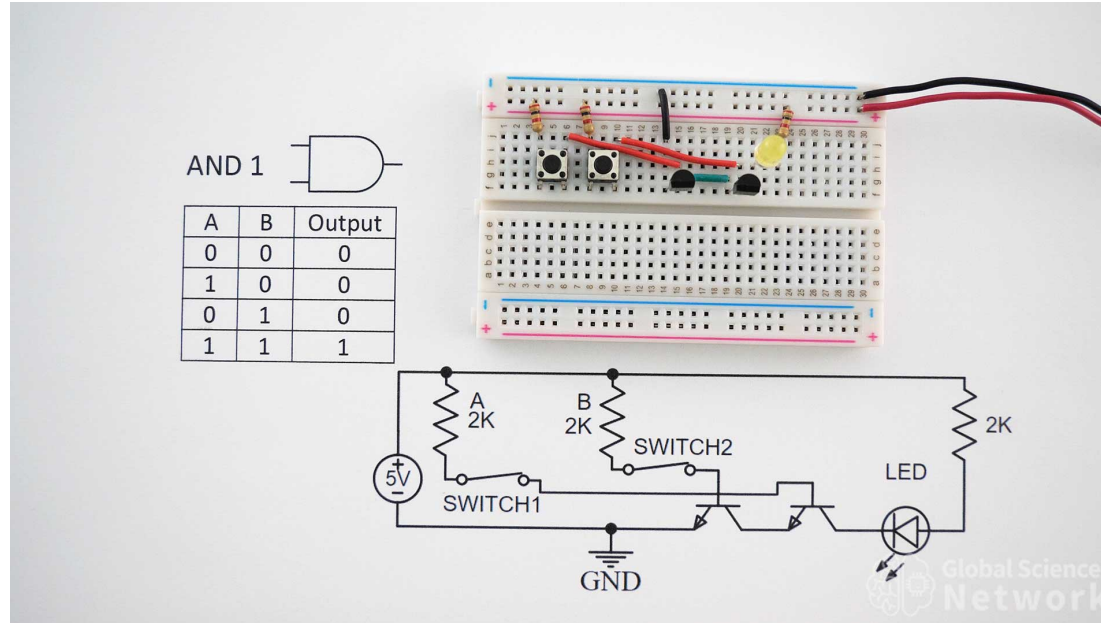


AND GATE CIRCUIT DIAGRAM

AND

 


$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 

SINGLE INPUT VS TWO INPUT GATES


NOT

 

$$Y = \overline{A}$$

A	Y
0	
1	

OR

 


$$Y = A + B$$

A	B	Y
0	0	
0	1	
1	0	
1	1	

MORE LOGIC GATES


XOR

 

$$Y = A \oplus B$$

A	B	Y
0	0	
0	1	
1	0	
1	1	


NAND

 

$$Y = \overline{AB}$$

A	B	Y
0	0	
0	1	
1	0	
1	1	


NOR

 

$$Y = \overline{A + B}$$

A	B	Y
0	0	
0	1	
1	0	
1	1	



XNOR

 



$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	
0	1	
1	0	
1	1	

NPN (NMOS) VS PNP (PMOS) TRANSISTORS

  

nMOS

  




pMOS

NMOS VS PMOS




$g = 0$

$g = 1$

nMOS

   


pMOS

   


PULL UP PULL DOWN NETWORKS

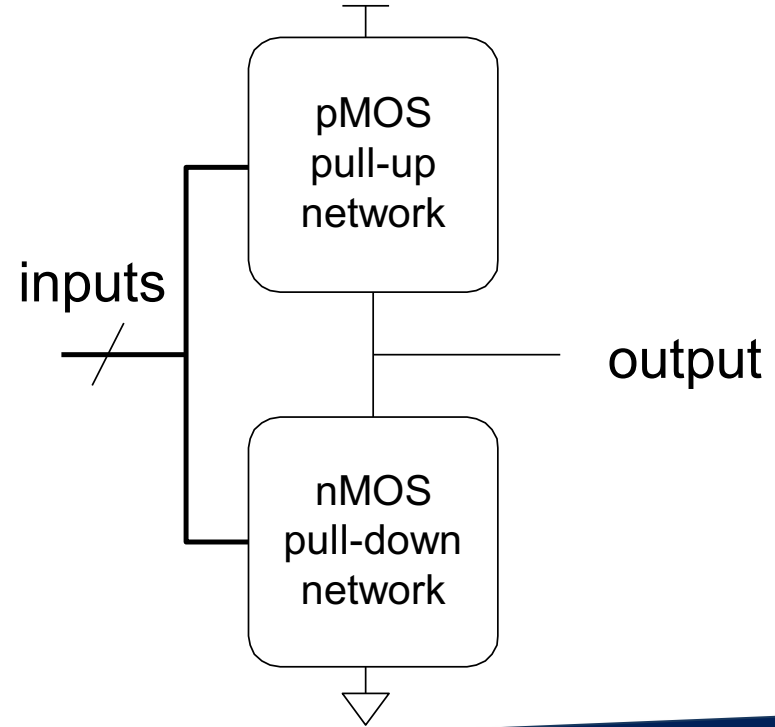- **nMOS**: pass good **0**'s, so connect source to GND
- **pMOS**: pass good **1**'s, so connect source to V_{DD}




NOT GATE

NOT

 


$$Y = \overline{A}$$

<i>A</i>	<i>Y</i>
0	1
1	0

 


<i>A</i>	<i>P1</i>	<i>N1</i>	<i>Y</i>
0			
1			


NAND

 

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 


 


<i>A</i>	<i>B</i>	P1	P2	N1	N2	<i>Y</i>
0	0					
0	1					
1	0					
1	1					

WHAT IS THE OUTPUT OF
THIS CIRCUIT?

A	B	C	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 


EXPRESS CIRCUIT AS AN EQUATION

 

Write the equation representing the circuit. Note I replaced the OR with a NOR.

EXAM QUESTION

 

SPRING 2022
Midterm 1

Fill in the following truth table for this circuit:

A	B	C	D
0	0	0	
0	0	1	
0	1	0	
0	1	1	

CREATIVE QUESTIONS

NAND GATES ARE TURNING COMPLETE


It is possible to implement every other gate by using a NAND. You can implement the complete RISC-V architecture using only NAND gates. What a beautiful building block right 😊

Hint: Start by asking NOT what a NAND gate can do for you but what you can do with a NAND gate.


Use a NAND gate to implement the following gates:

1. NOT
2. AND
3. OR
4. NOR
5. XOR


NAND Gate Symbol

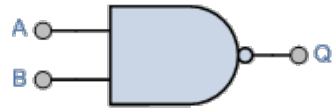


NOT Gate
(Inverter)

 


AND Gate

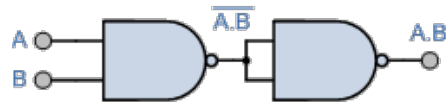


Buffer

 


OR Gate

 

Exclusive-OR

 

NOR Gate

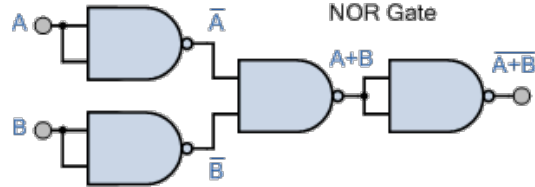

Exclusive-NOR

