

COMPUTER SYSTEMS AND ORGANIZATION

Part 1


Daniel Graham




UNIVERSITY
of VIRGINIA

ENGINEERING

REVIEW

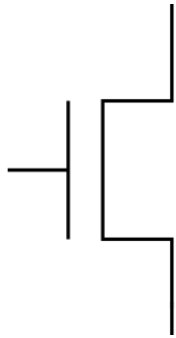


push to close

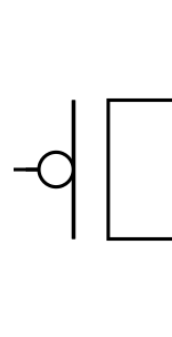


push to open

NAND

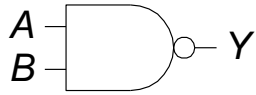


$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

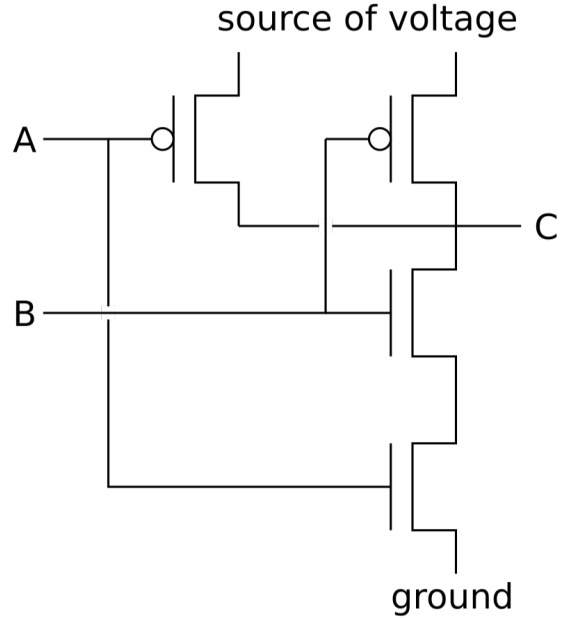


NAND

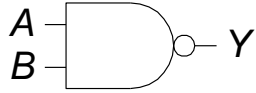

$$Y = \overline{AB}$$


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Source of Voltage (VDD)

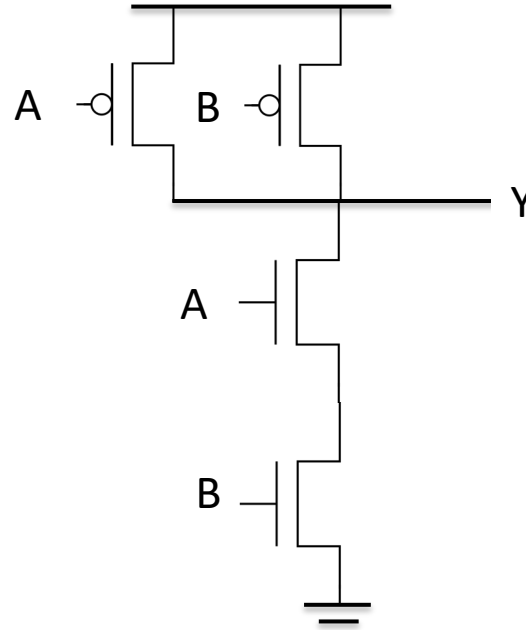


Ground


NAND

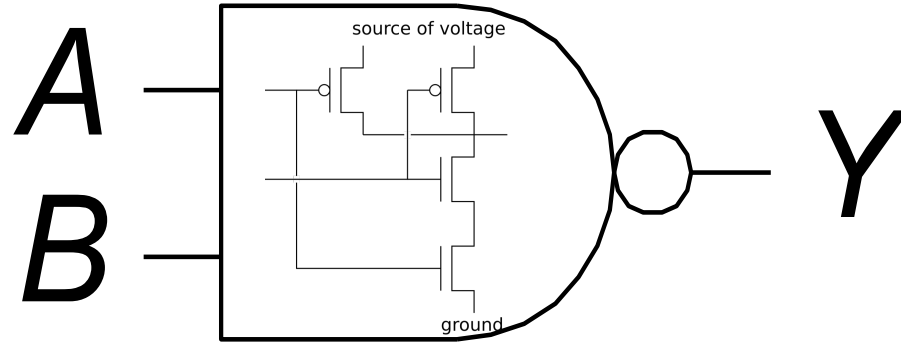

$$Y = \overline{AB}$$



Circuit with a NAND Gate

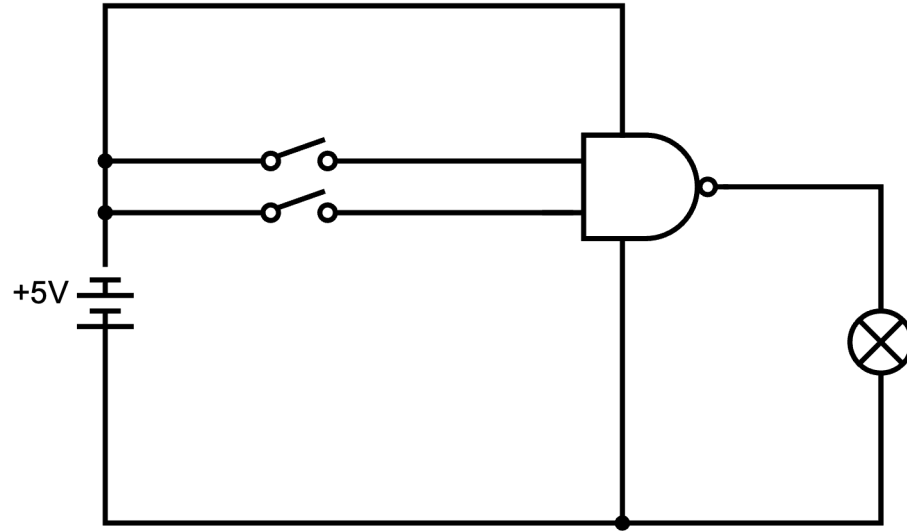

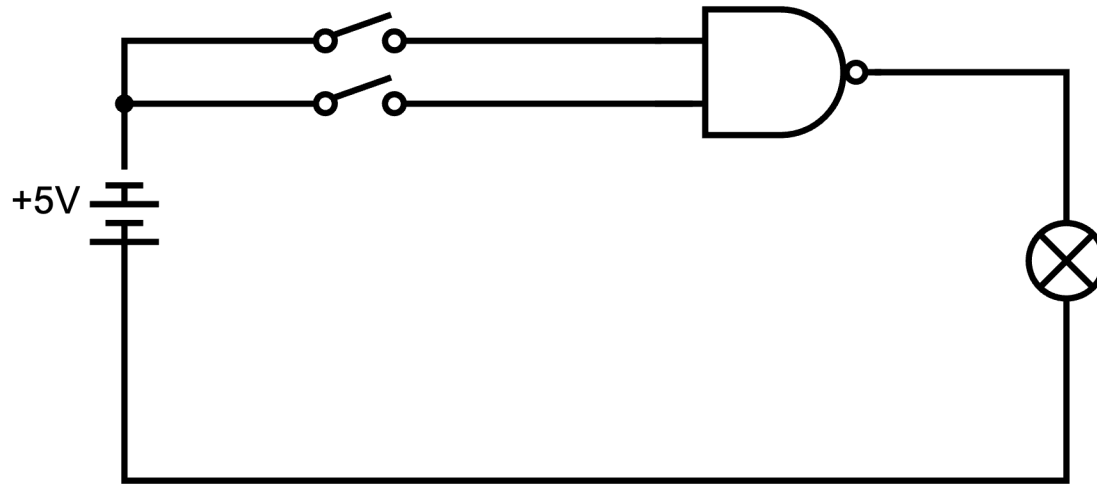

We don't normally draw the voltage and ground with gates. So you will normally see circuits that look like this.

CHIPS WITH NAND GATES

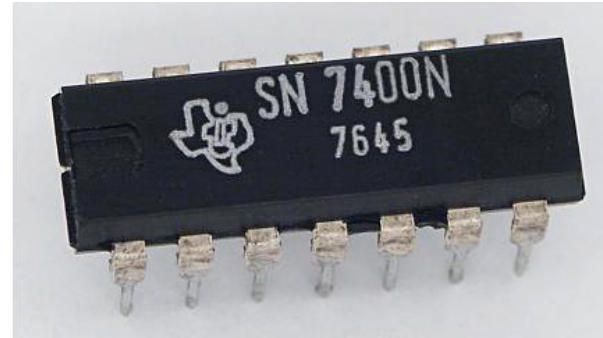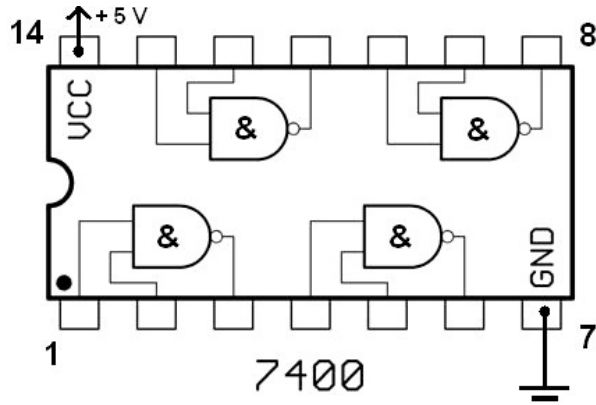

Untitled* x

DESIGN DOCUMENT VALIDATE AUTOMATE LIBRARY

SWITCH VIEW EDIT PLACE CONNECT SIMULATE REWORK MODIFY SHORTCUTS SELECT

DESIGN MAN... DISPLAY LA... ERR... PLACE COMPO... 91 Nets 0.1 inch (5.2 1.5) Click or press / to activate command line mode

All Libraries

led

Compo...	Library	Variant
ACSAS...	Dis...	
CAT36...	IC...	TQFN16
CHIP...	LED	_0402
CHIP...	LED	_0402
CHIP...	LED	_0402
CHIP...	LED	_0402
CHIP...	LED	_1209
CHIP...	LED	_1209
CHIP...	LED	_1209
CHIP...	LED	_1209
CPC99...	IC...	E
D*04-1...	Dis...	
D*7SU...	Dis...	S6-51
DA03...	Dis...	
E-L625...	IC...	POWER_SO-36
HV993...	IC...	LG
HV996...	IC...	LG/TG
LED_C...	Opt...	RED-3216
LED_C...	TuL...	RED-2012
LED_R...	Opt...	YELLOW
PD*54...	Dis...	"
TLC591...	IC...	TSSOP
WS2812	LED	
WS281...	LED	

30 Components

Details Attributes

CHIP-FLAT-B_0402

G81 >NAME >VALUE

>NAME >VALUE

Net: N\$1, Class: 0 default |

NET

Name: Auto-generated

Auto-generate: ☒

Loop:

Net Class: 0 default

Done

Inspector

Selection Filter

DESIGN DOCUMENT RULES DRC/ERC MANUFACTURING AUTOMATION SIMULATION LIBRARY
 SWITCH VIEW EDIT LAYERS BOARD SHAPE PLACE ROUTE QUICK ROUTE POLYGON UNROUTE REWORK MODIFY SHORTCUTS SELECT

DISPLAY LAYERS ERRORS PLACE COMPONENTS DESIGN MANAGER
 1 Top 50 mil (732 1153) Click or press / to activate command line mode

Browser Filter
 Assembly Variant: Default Variant
 View: Components
 Component Sets 3 of 3 shown (1 selected)
 Search
 Component Set
 <All Components>
 <Bottom Side Components>
 <Top Side Components>

Components 5 of 5 shown (0 selected)
 Search

Jam	Device	Footprint	Val
BT1	(796136-1)	796136-1	796136
D1	_0402 (CHIP-FLAT-B)	LEDC1005X25N_FLAT-B	LED_BIL
IC1	_PDIP (74HC00)	DIP762W53P254L1969H508Q14B	74HC00
S1	(DS01E)	DS-01	DS01E
S2	(DS01E)	DS-01	DS01E

Items 0 of 0 shown (0 selected)
 Search

Type	Name	Signal	Layer	Size
------	------	--------	-------	------

DESIGN DOCUMENT RULES DRC/ERC MANUFACTURING AUTOMATION SIMULATION LIBRARY

SWITCH VIEW LAYERS ANNOTATE OUTPUTS DRAW ATTRIBUTES

DISPLAY LAYERS ERRORS PLACE COMPONENTS DESIGN MANAGER

1 Top 50 mil (-513 1009) Click or press / to activate command line mode

Assembly Variant: Default Variant

View: Components

Component Sets 3 of 3 shown (1 selected)

Search

Component Set

- <All Components>
- <Bottom Side Components>
- <Top Side Components>

Components 5 of 5 shown (0 selected)

Search


Item	Device	Footprint	Value
BT1	(796136-1)	796136-1	796136-1
D1	_0402 (CHIP-FLAT-B)	LEDC100SX25N_FLAT-B	LED_BLUE
IC1	_PDIP (74HC00)	DIP762W53P254L1969H508Q14B	74HC00
S1	(DS01E)	DS-01	DS01E
S2	(DS01E)	DS-01	DS01E


Items 0 of 0 shown (0 selected)

Search

Type	Name	Signal	Layer	Size
------	------	--------	-------	------


CS 2130 NAND GATE BOARD

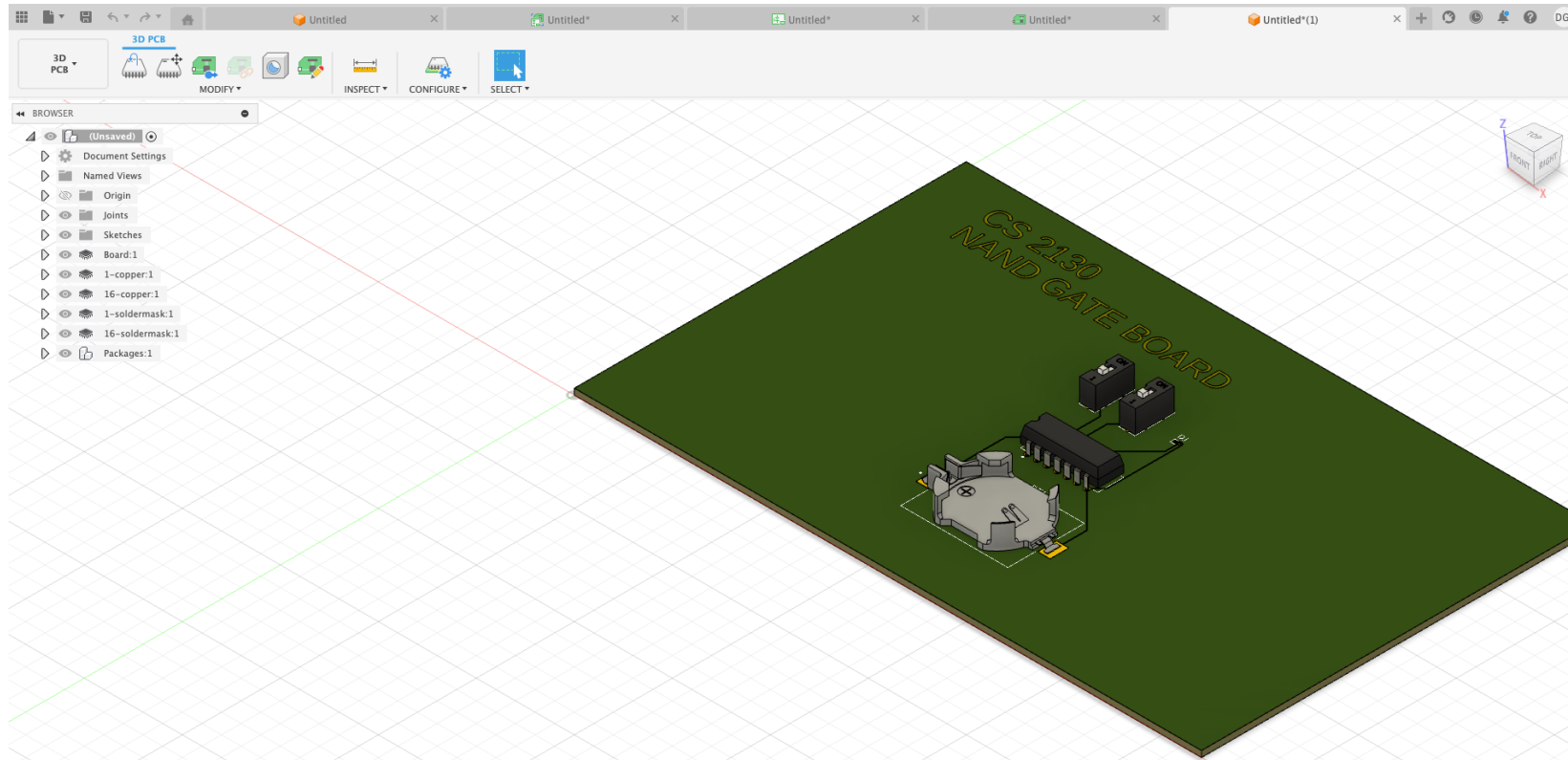

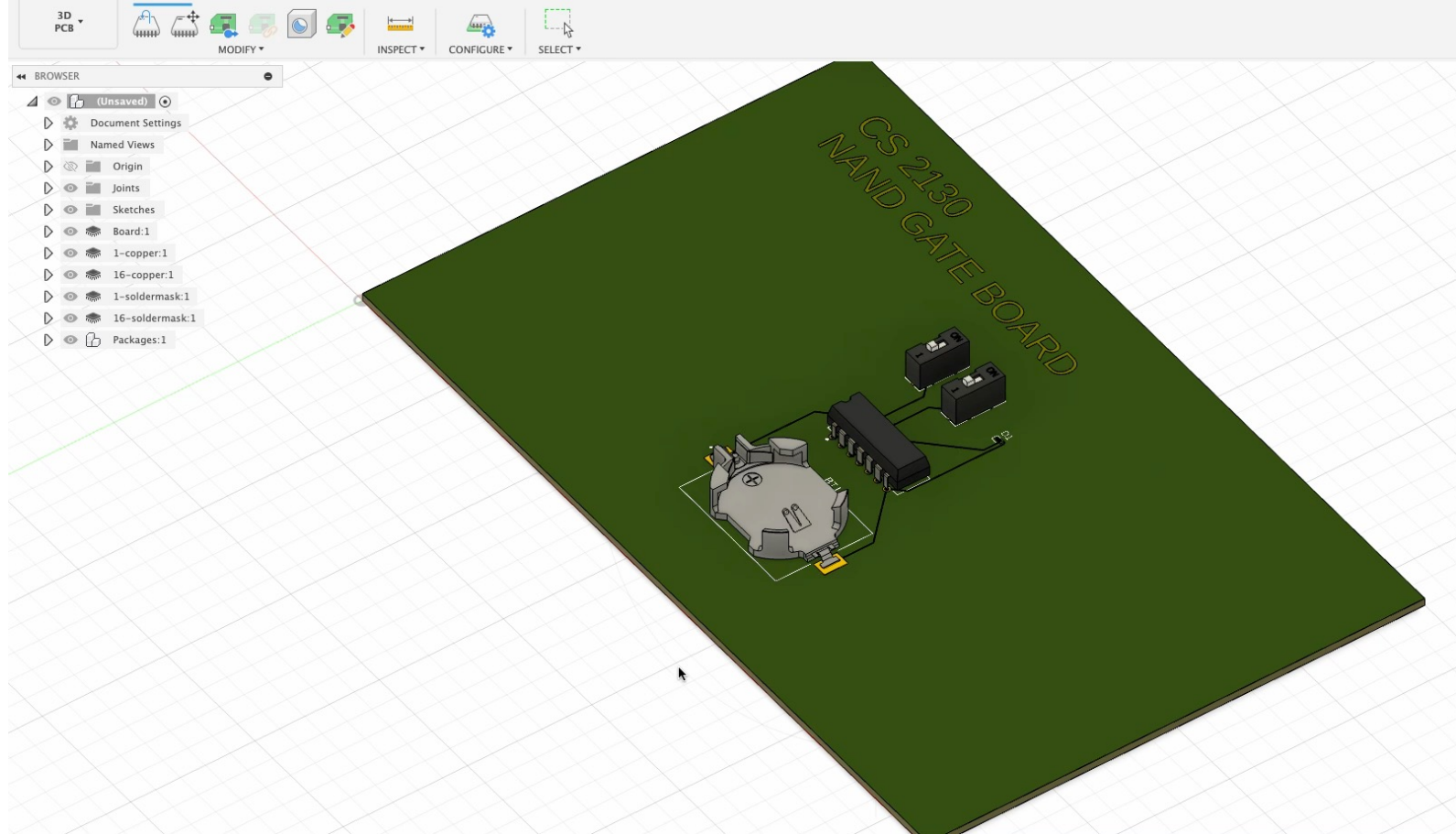


WHAT IS THE OUTPUT OF
THIS CIRCUIT?

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

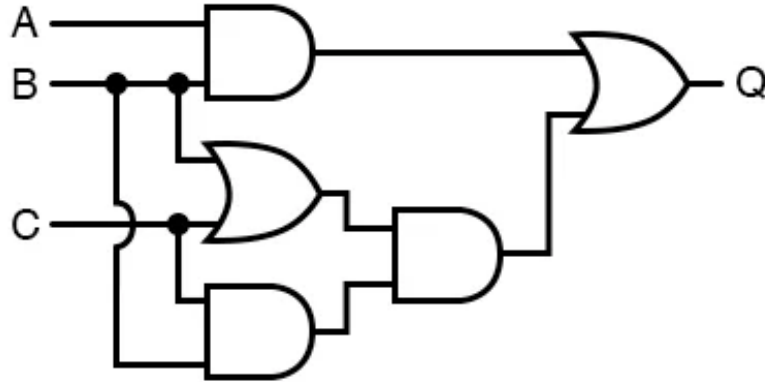


EXPRESS CIRCUIT AS AN EQUATION

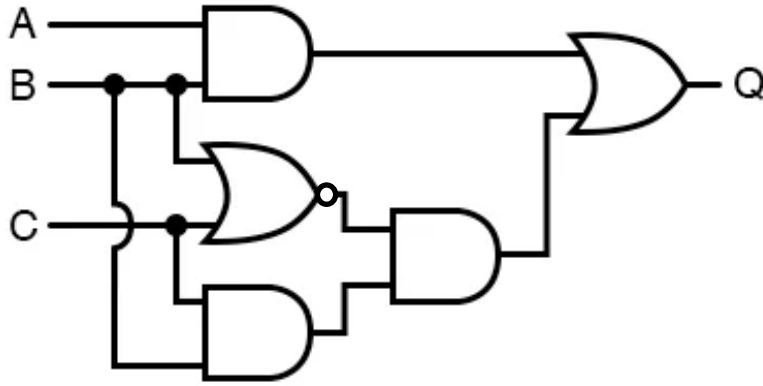

Write the equation representing the circuit. Note I replaced the OR with a NOR.

EXAM QUESTION

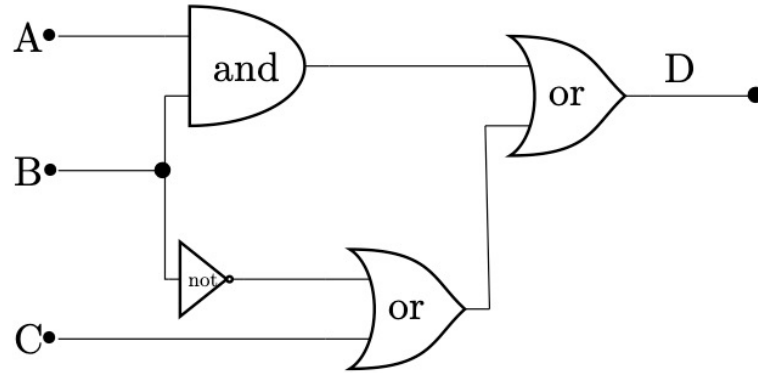

SPRING 2022
Midterm 1

Fill in the following truth table for this circuit:

A	B	C	D
0	0	0	
0	0	1	
0	1	0	
0	1	1	

CREATIVE QUESTIONS

NAND GATES ARE TURNING COMPLETE


It is possible to implement every other gate by using a NAND. You can implement the complete RISC-V architecture using only NAND gates. What a beautiful building block right 😊

Hint: Start by asking NOT what a NAND gate can do for you but what you can do with a NAND gate.


Use a NAND gate to implement the following gates:

1. NOT
2. AND
3. OR
4. NOR
5. XOR


NAND Gate Symbol

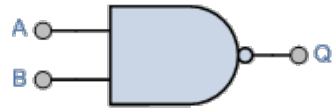


NOT Gate
(Inverter)

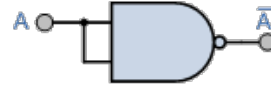


AND Gate

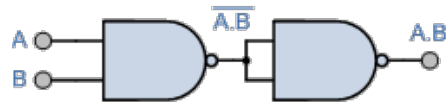


Buffer

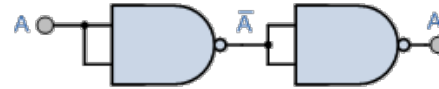


OR Gate

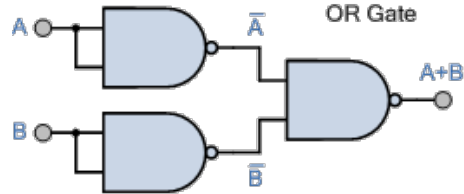


Exclusive-OR

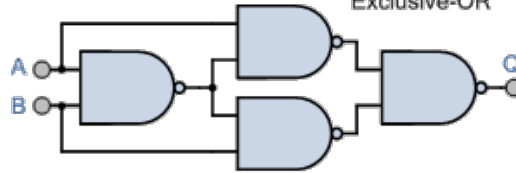

NOR Gate

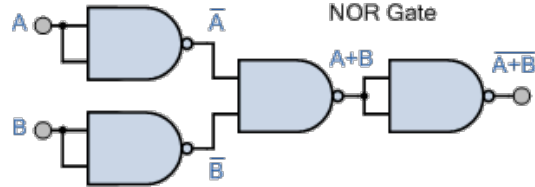

Exclusive-NOR

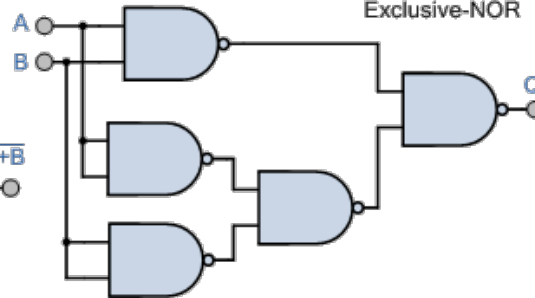


TODAY'S LECTURE



1. Building Component out of gates. (Muxes a case study)
2. Towards building a digital adding machine
3. How can we represent numbers? (What about decimals and negative numbers)

MUXES


Example: 2:1 Mux

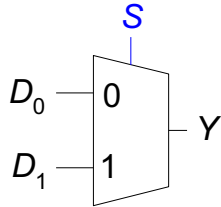

S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		

- Selects between one of N inputs to connect to output
- **Select** input is $\log_2 N$ bits – control input


1 BIT MUX

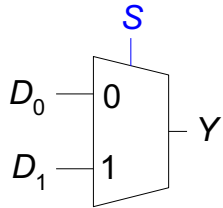



S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

S	Y
0	D_0
1	D_1



$$Y = D_0 \bar{S} + D_1 S$$

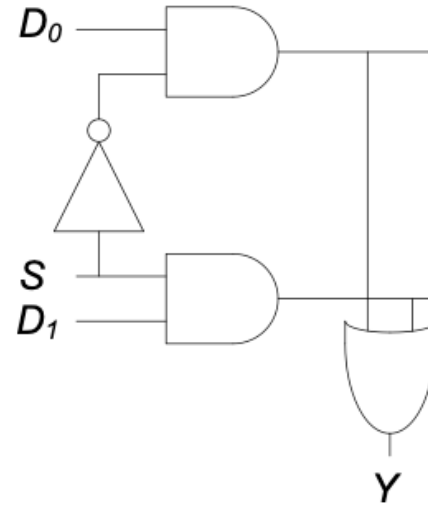

2 BIT MUX

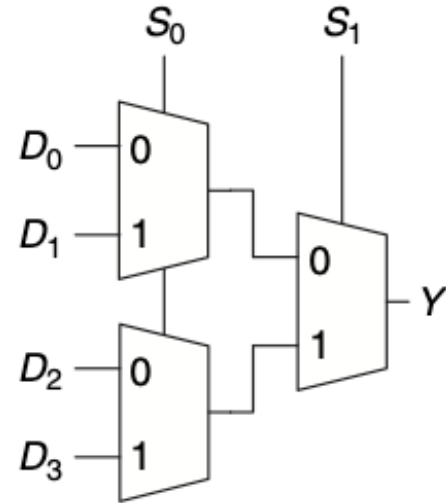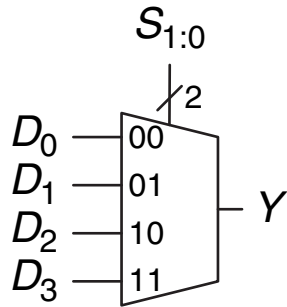

2 BIT MUX

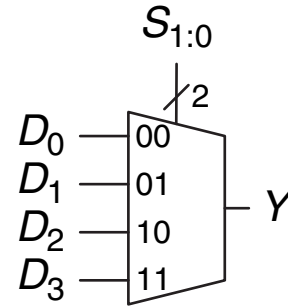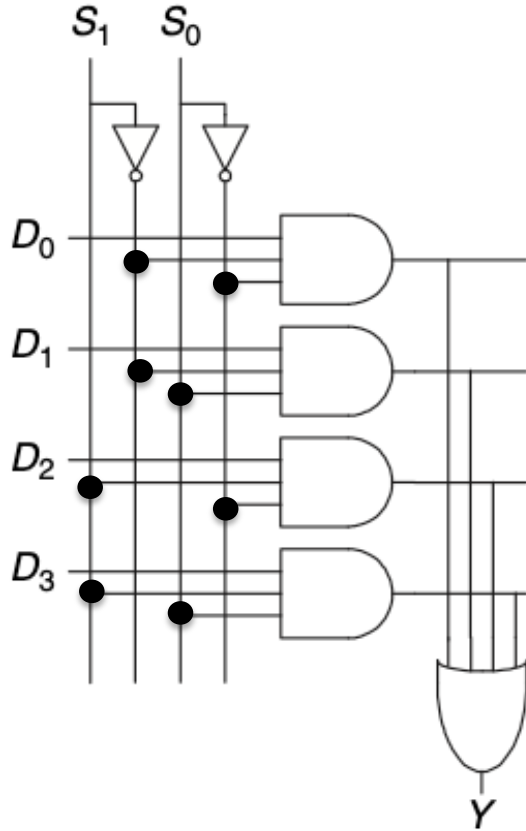


MUX AS A LOOK UP TABLE

Using mux as a **lookup table**


A	B	Y
0	0	0
0	1	1
1	0	0
1	1	0

$$Y = AB$$

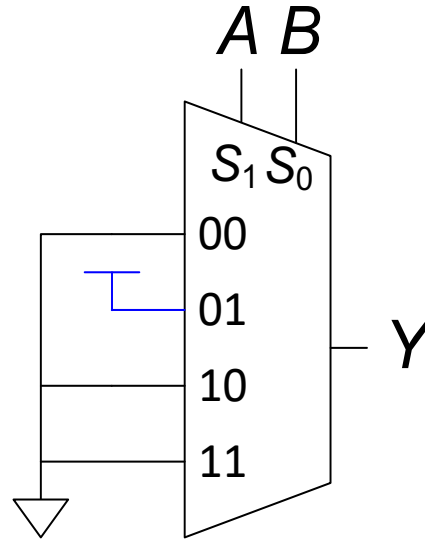

GREAT WE HAVE GATES
NOW LET'S BUILD SOMETHING.
HOW ABOUT A MACHINE THAT ADDS
NUMBERS?

THE IDEA

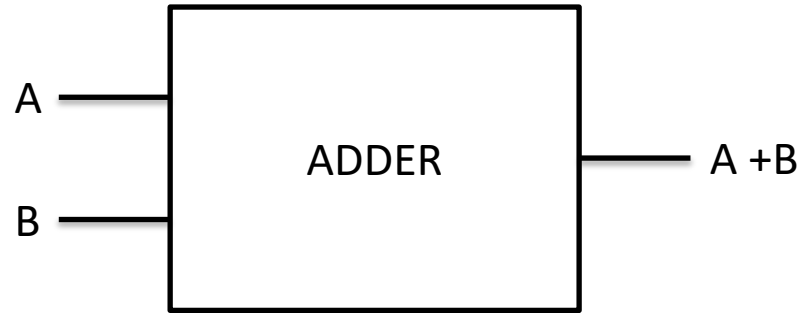

THE CHALLENGE

Our gates only support 0 and 1s.

How can we represent other decimal numbers?

How can we present negative numbers?

What about fractions 😊?

DECIMAL

- Decimal numbers

1's column
10's column
100's column
1000's column

$$5374_{10} = 5 \times 10^3 + 3 \times 10^2 + 7 \times 10^1 + 4 \times 10^0$$

five thousands three hundreds seven tens four ones


BINARY


1's column
2's column
4's column
8's column

$$1101_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 13_{10}$$

one eight one four no two one one

4-BIT ADDER

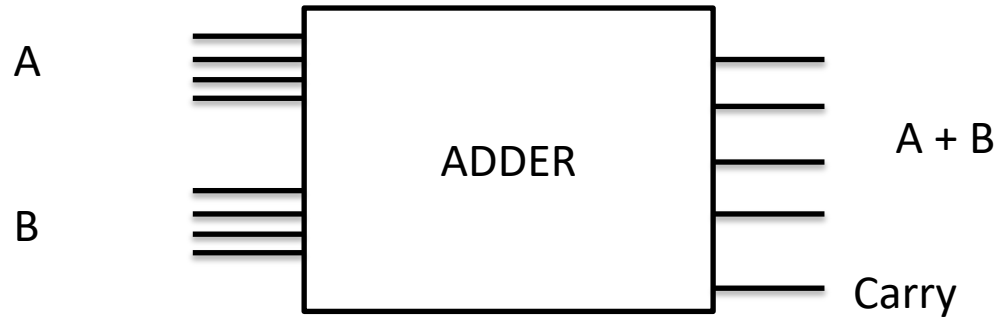

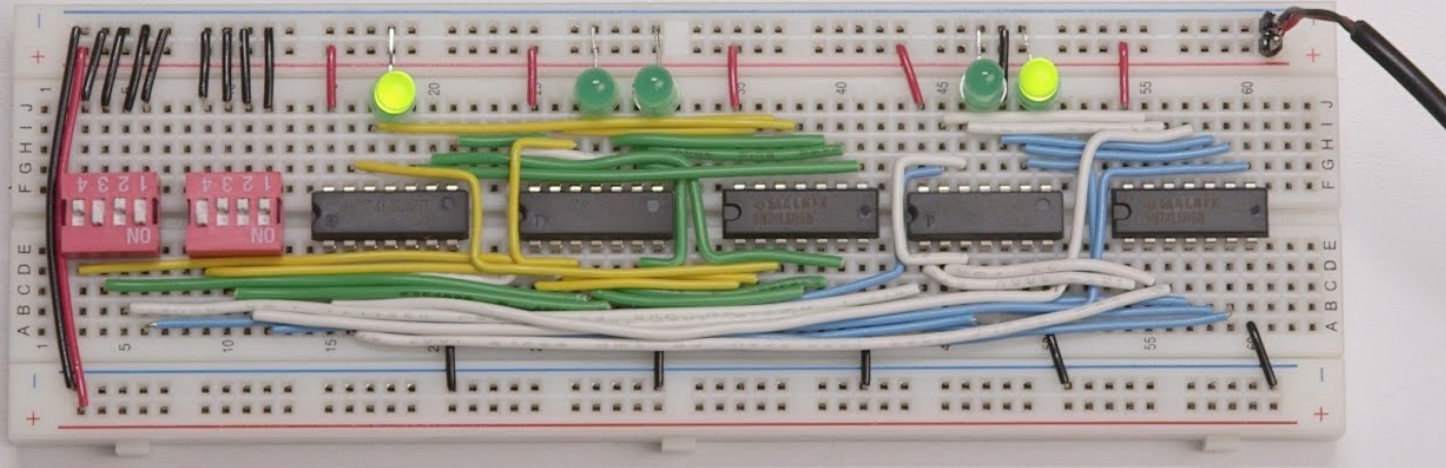

How do computers add numbers?

INPUTS AND OUTPUT OF OUR ADDER


What would the input be if wanted to add 5, and 9?

Notice we need to pick and order for the wires. More on this later 😊

Which output lights would we want to light Up?

A


B

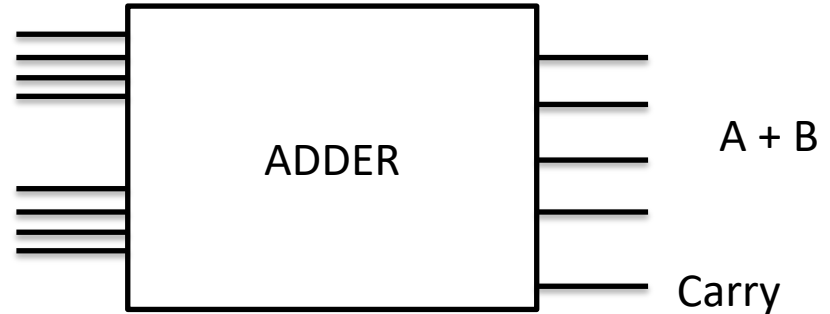


INPUTS AND OUTPUT OF OUR ADDER

What if we now added 7 and 9?

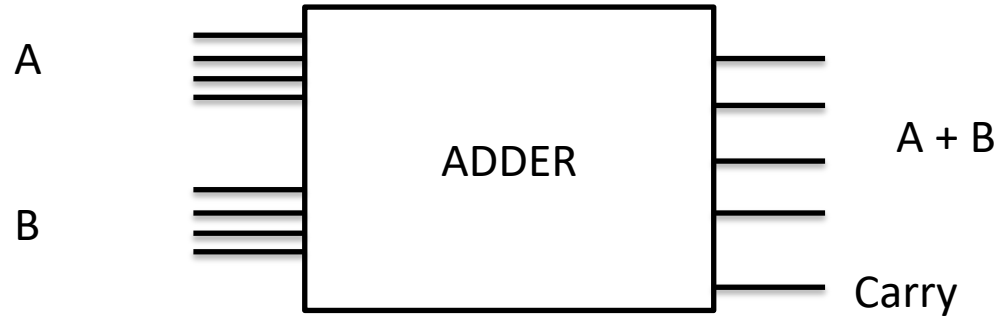What would our inputs be and which lights do we expect to light up?



WHAT ABOUT NEGATIVE NUMBERS

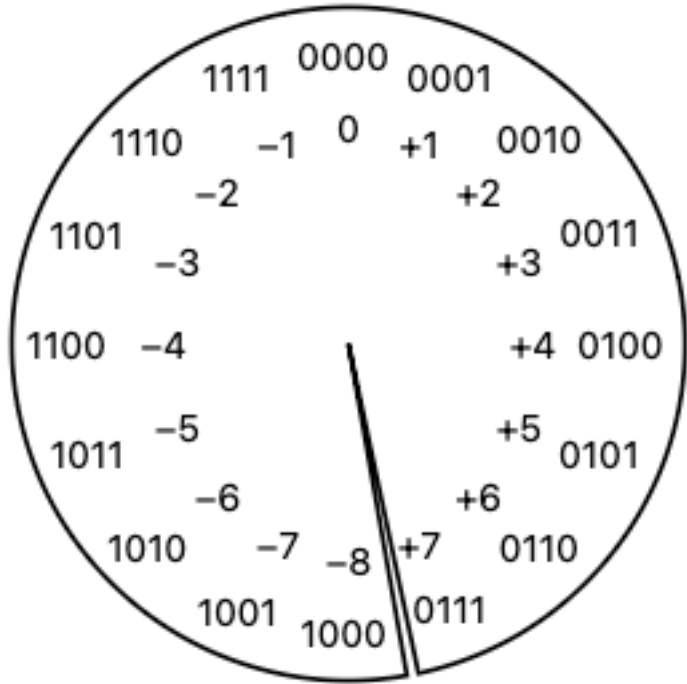

Two's complement picks a number (typically half of the maximum number we can write, rounded up) and decides that that number and all numbers bigger than it are negative

Two's complement is nice because the three most common mathematical operators (addition, subtraction, and multiplication) work the same for signed and unsigned values. Division is messier, but division is always messy

EXAM REVIEW FALL 2018

The following assume 8-bit 2's-complement numbers. For each number, bit 0 is the low-order bit, bit 7 is the high-order bit.

Question 2 [2 pt]: (see above) Complete the following sum, showing your work (carry bits, etc)

$$\begin{array}{r} 0\ 0\ 1\ 1\ 0\ 0\ 1\ 1 \\ +\ 0\ 1\ 1\ 0\ 0\ 1\ 1\ 0 \\ \hline \end{array}$$

What is the result in base 10? Is it negative or positive? Would you get the same result in decimal if you had more bits 😊 ?

WRITING LONG BINARY IS NO FUN.
LET'S EXPRESS IT IN ANOTHER BASE TO MAKE
EASIER. DEFINITELY CHOOSE SOMETHING
LARGER THAN BASE 10

HEXADECIMAL

Hex Digit	Decimal	Binary
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

